 


Discussion 13


Timing, FF/Latch Design, SRAMs, Caches

Latch Timing




- A positive latch is transparent ($q = d$) when the clock is high and opaque ($q = d$, during negedge clock) when the clock is low
- $t_{d \rightarrow q}$ is the delay from d to q when the latch is transparent
- $t_{clk \rightarrow q}$ is the delay from the rising clock edge to d propagating to q


Latch Circuits

 

 ‘Feedback-breaking’ latch
Transparent high




‘State-forcing’ latch
Transparent low

 

S	R	Q	\bar{Q}
0	0	latch	latch
0	1	0	1
1	0	1	0
1	1	0	0


SR latch
Common interview question

Building a Flip-Flop from Latches

 

- Clock pulsed latch
 - Latch becomes transparent for a short time and holds the value it received on the pulse
 - Not common anymore, sometimes used in high performance circuits
 - Positive hold time
- Master-slave latches
 - Commonly used technique. L2 holds output data stable when clock is high. L2
 - Negative hold time

Flip-Flop Hold/Setup/clk→q Time

 

- This is a negative edge flip-flop as drawn
- We'll consider the positive edge case

- Hold time = the amount of time after a clock edge that the data input needs to be stable for (can be negative)
- Setup time = the amount of time before a clock edge that the data input needs to be stable to be properly latched internally
- Clk-q time = delay from a clock edge to q being updated with the new value written


Path Timing Constraints

Setup constraint: $T_{\{clk\}} > t_{\{clk \rightarrow q\}} + t_{\{logic, max\}} + t_{\{setup\}}$

- The clock period must be greater than the delay of the critical path


Hold constraint: $t_{\{hold\}} < t_{\{clk \rightarrow q\}} + t_{\{logic, min\}}$

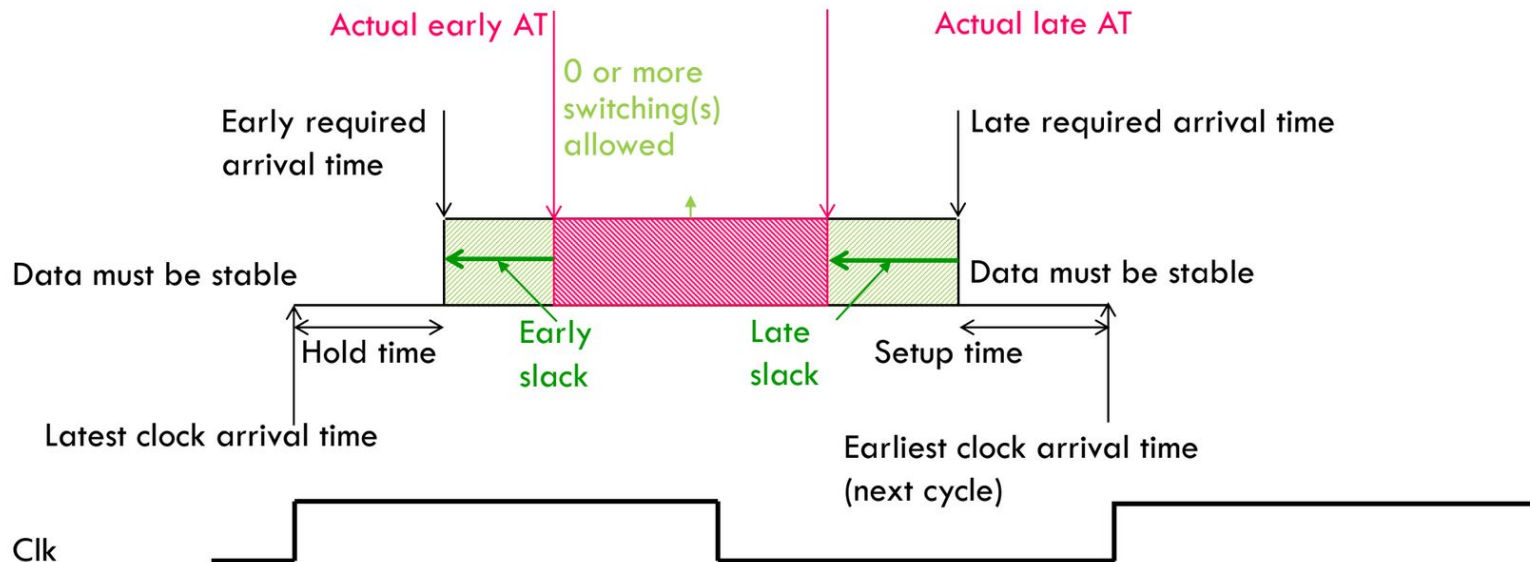- The minimum logic delay must be greater than the hold time



False Paths

 - Be careful about finding the critical path by statically adding up delays
- Some paths may not be exercised based on logic expressions
- Here, the critical path is 300ns, not 400ns



Clock Skew

Setup constraint: $T_{\{clk\}} > t_{\{clk \rightarrow q\}} + t_{\{logic,max\}} + t_{\{setup\}}$

Hold constraint: $t_{\{hold\}} < t_{\{clk \rightarrow q\}} + t_{\{logic,min\}}$


- Skew is the deterministic clock arrival time difference between 2 flops
- Positive skew = receiving edge arrives later than nominal
- Negative skew = receiving edge arrives earlier than nominal
- New timing equations:
 - $T_{\{clk\}} > t_{\{clk \rightarrow q\}} + t_{\{logic,max\}} + t_{\{setup\}} - t_{\{skew\}}$
 - Note positive skew can improve clock frequency
 - Negative skew hurts setup margin
 - $t_{\{hold\}} + t_{\{skew\}} < t_{\{clk \rightarrow q\}} + t_{\{logic,min\}}$
 - Note positive skew hurts hold margin

Clock Jitter

- Jitter is the non-deterministic difference in clock arrival times
 - Can be treated like skew in timing calculations
 - Assuming worst case jitter in the unfavorable direction for each timing calculation
 - Can lump the jitter of both the launching and receiving FFs into an equivalent skew

SRAM Architecture

 
- CORE
 - Wordlines to access rows
 - Bitlines to access columns
 - Data multiplexed onto columns
- Decoders
 - Addresses are binary
 - Row/column MUXes are 'one-hot' - only one is active at a time




- SRAM bitcells arranged in a grid
- Bitlines (vertical) are shared across cells in a column, they are often long wires with a large capacitive load (connect to drains of access transistors)
- Wordlines (horizontal) are shared across cells in a row, they connect to the gates of access transistors
- Peripheral circuitry (bitline drivers, sense amp, decoders)

6T SRAM Cell

 
- Inverters in positive feedback form the memory element (similar to a latch)
- M5/M6 are the access transistors; they allow the bitlines to access the memory nodes (Q, Qbar) when $WL = 1$
- Only 1 WL in an SRAM array is active at a time and it addresses an entire row of SRAM cells
- Bitlines are controlled differently for read and write



6T SRAM Cell - 3 Modes of Operation

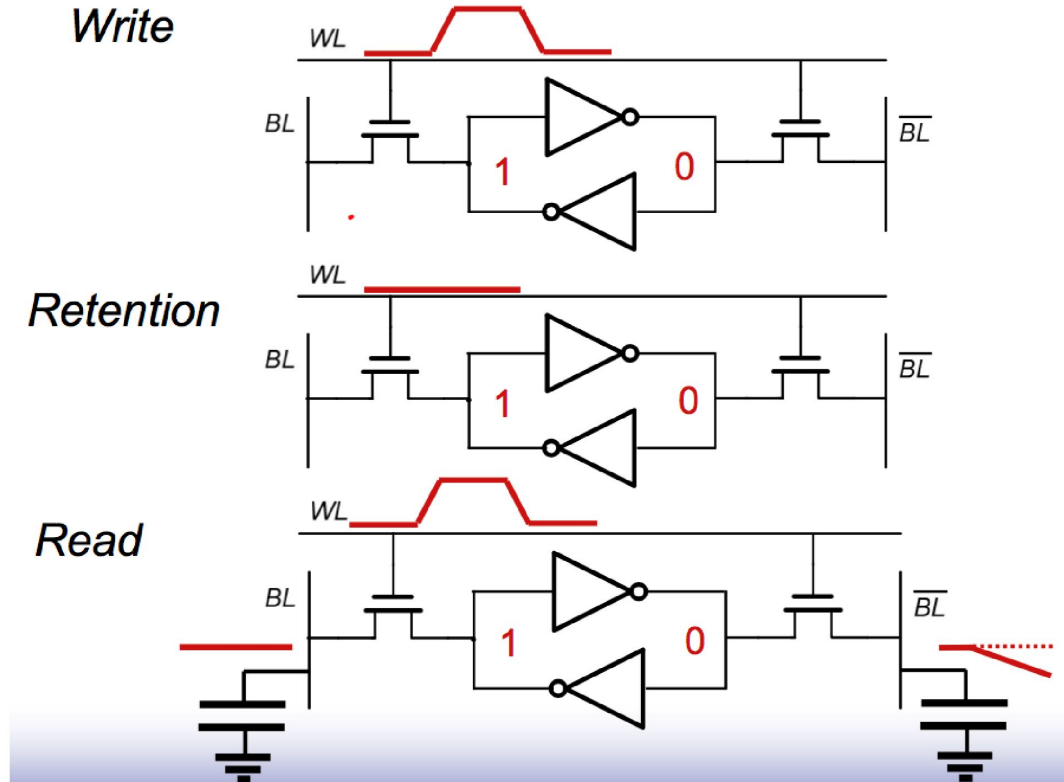


SRAM Read

 

- 1) precharge BL and BLbar to VDD, 2) raise WL, 3) sense dip on one bitline with sense amp, 4) lower WL, 5) discharge bitlines
- Read stability = reading doesn't corrupt the value stored in Q and Qbar
 - The pass transistor shouldn't overpower the node storing a '0' and flip its state (consider voltage divider from bitline to Q)
- We choose to make the NMOSes in the inverters stronger than the pass transistor = ($W_n > W_{pass}$) to prevent read corruption


SRAM Write

Write

 


- 1) drive BL and BLbar with new values, 2) raise WL, 3) wait some time (write time), 4) lower WL, 5) discharge bitlines
- Write-ability = the cell's memory value can be changed
 - requires the pass transistor overpower one of the data nodes
 - If we assume the cell is read stable, the inverter NMOS is stronger than the pass transistor. This means the node with '0' can't be overpowered => so we *must overpower PMOS*.
- Pass transistor strength > PMOS pullup strength = ($W_{pass} > W_p$)
 - Voltage divider on '1' node must be strong enough to cause inverters to switch

Caches - Direct Mapped

 

Caches - N-Way Set Associative

 

Caches - Fully Associative

