

EECS151 : Introduction to Digital Design and ICs

Lecture 19 – Caches


Bora Nikolić and Sophia Shao



Have you ever wondered where escaping party balloons go to?

Nov. 14, 2019. Students in EE-84 class taught by Prof. Miki Lustig launched a balloon equipped with a transponder and GPS+solar cells+super capacitors, can be tracked:
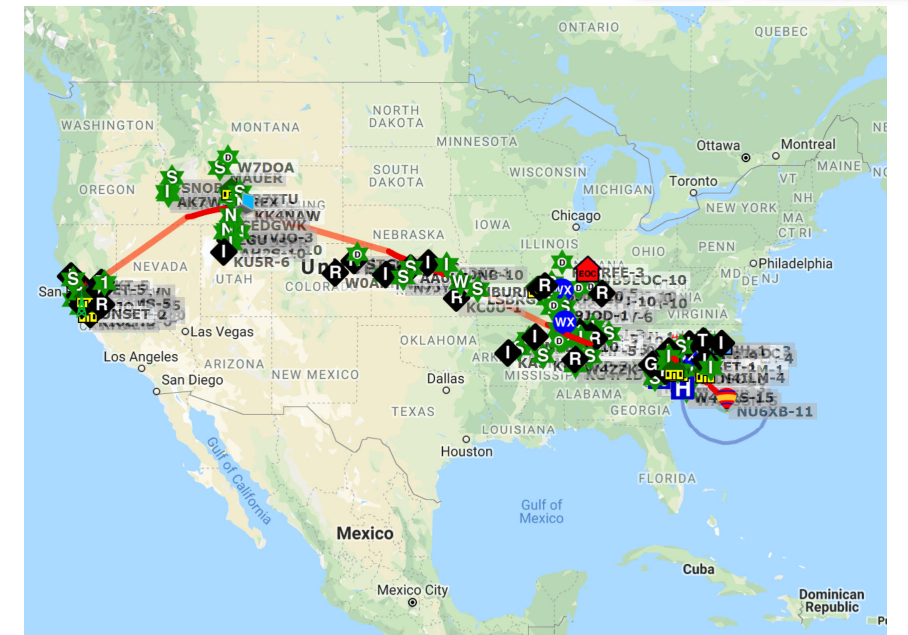
<https://aprs.fi/#!mt=roadmap&z=8&call=a%2FNU6XB11&timerange=604800&tail=604800>



Review

- Flip-flop is typically a latch pair
- Setup and hold times are defined at constant percentage increases over clk-q delay
- SRAM has unique combination of density, speed, power
- SRAM cells sized for stability and writeability





Multi-Ported SRAM

Multi-Ported Memory

- Motivation:
 - Consider CPU core register file:
 - 1 read or write per cycle limits processor performance.
 - Complicates pipelining. Difficult for different instructions to simultaneously read or write regfile.
 - Single-issue pipelined CPUs usually needs 2 read ports and 1 write port (2R/1W).
 - Superscalar processors have more (e.g. 6R/3W)


– I/O data buffering:

  


- dual-porting allows both sides to simultaneously access memory at full bandwidth.

Dual-Ported Memory Internals

 - Add decoder, another set of read/write logic, bits lines, word lines:




- Example cell: SRAM

 

- Repeat everything but cross-coupled inverters.
- This scheme extends up to a couple more ports, then need to add additional transistors.

1R/1W 8T SRAM

8-T SRAM

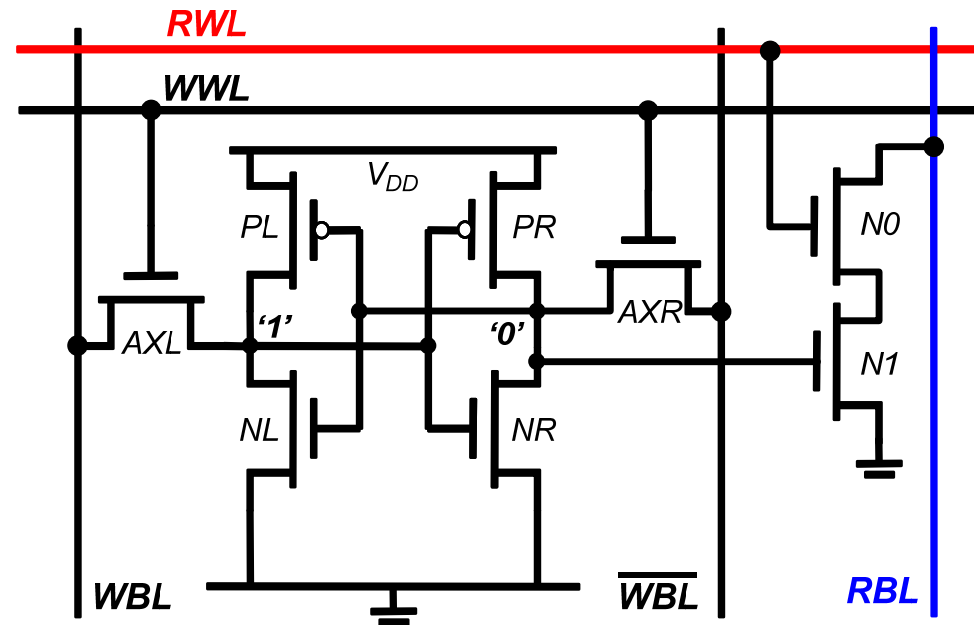

- Dual-port read/write capability
- Single-cycle read and write, timed appropriately
- Often found in register files, first level (L1) of cache

True or False

www.yellkey.com/could


1	F	F	F
2	F	F	T
3	F	T	F
4	F	T	T
5	T	F	F
6	T	F	T
7	T	T	F
8	T	T	T

1. Transistor leakage doesn't affect SRAM read speed
2. One should write into an SRAM cell by pulling BL high
3. One can only write into a part of a selected WL




Memory Decoders

Decoders

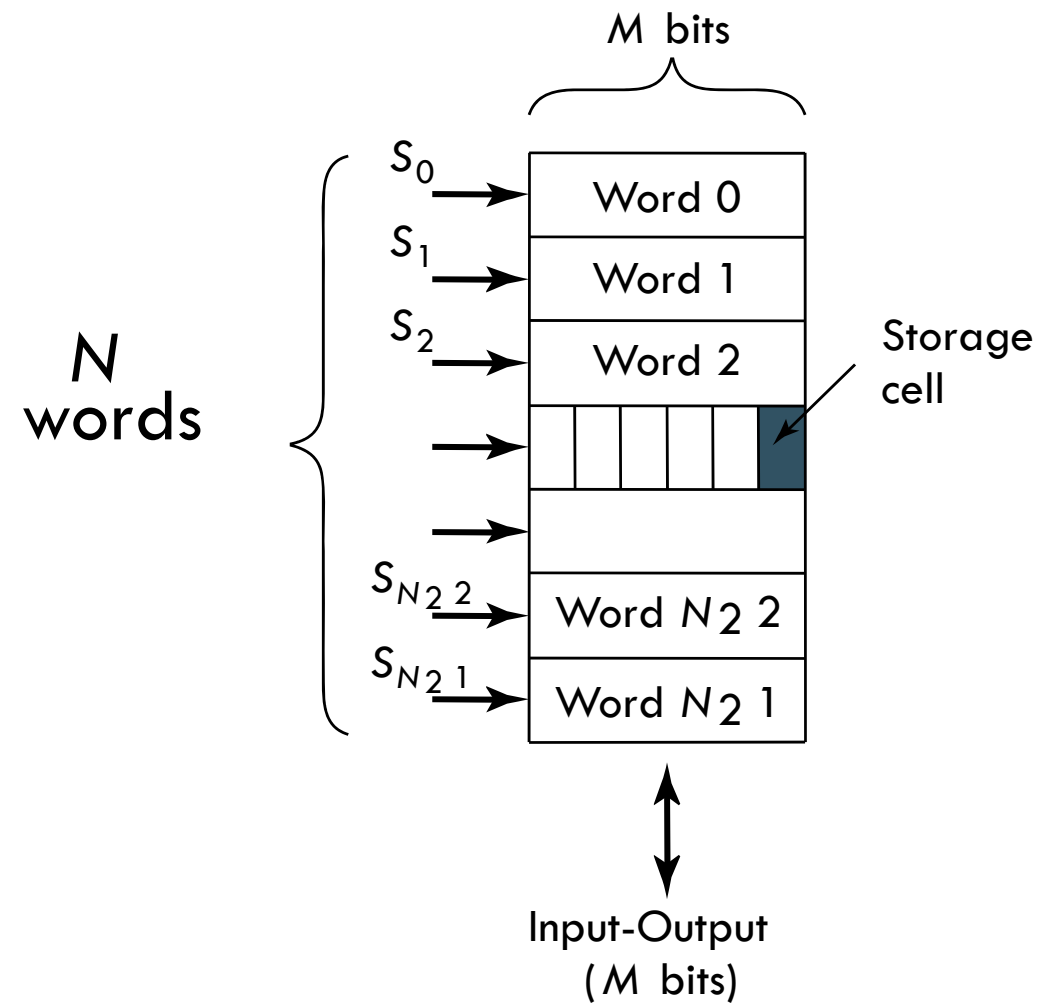

 Intuitive architecture for $N \times M$ memory
Too many select signals:
 N words = N select signals



Decoder reduces the number of select signals
 $K = \log_2 N$


Row Decoders

Collection of 2^M complex logic gates
Organized in regular and dense fashion

(N)AND Decoder

$$WL_0 = \overline{A_0} \overline{A_1} \overline{A_2} \overline{A_3} \overline{A_4} \overline{A_5} \overline{A_6} \overline{A_7} \overline{A_8} \overline{A_9}$$
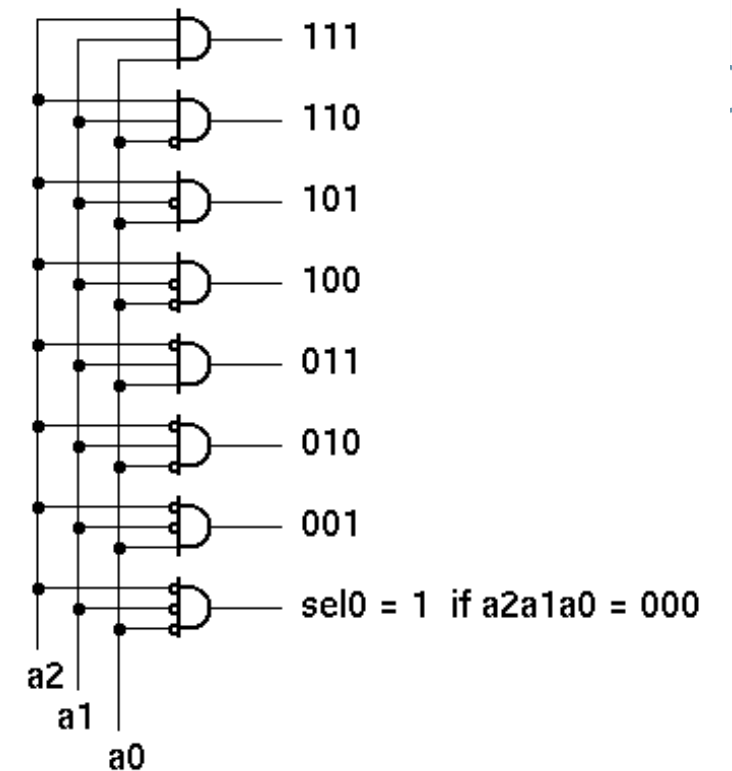
$$WL_{511} = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 \overline{A_9}$$




NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{\overline{A_0} + \overline{A_1} + \overline{A_2} + \overline{A_3} + \overline{A_4} + \overline{A_5} + \overline{A_6} + \overline{A_7} + \overline{A_8} + A_9}$$


Decoder Design Example

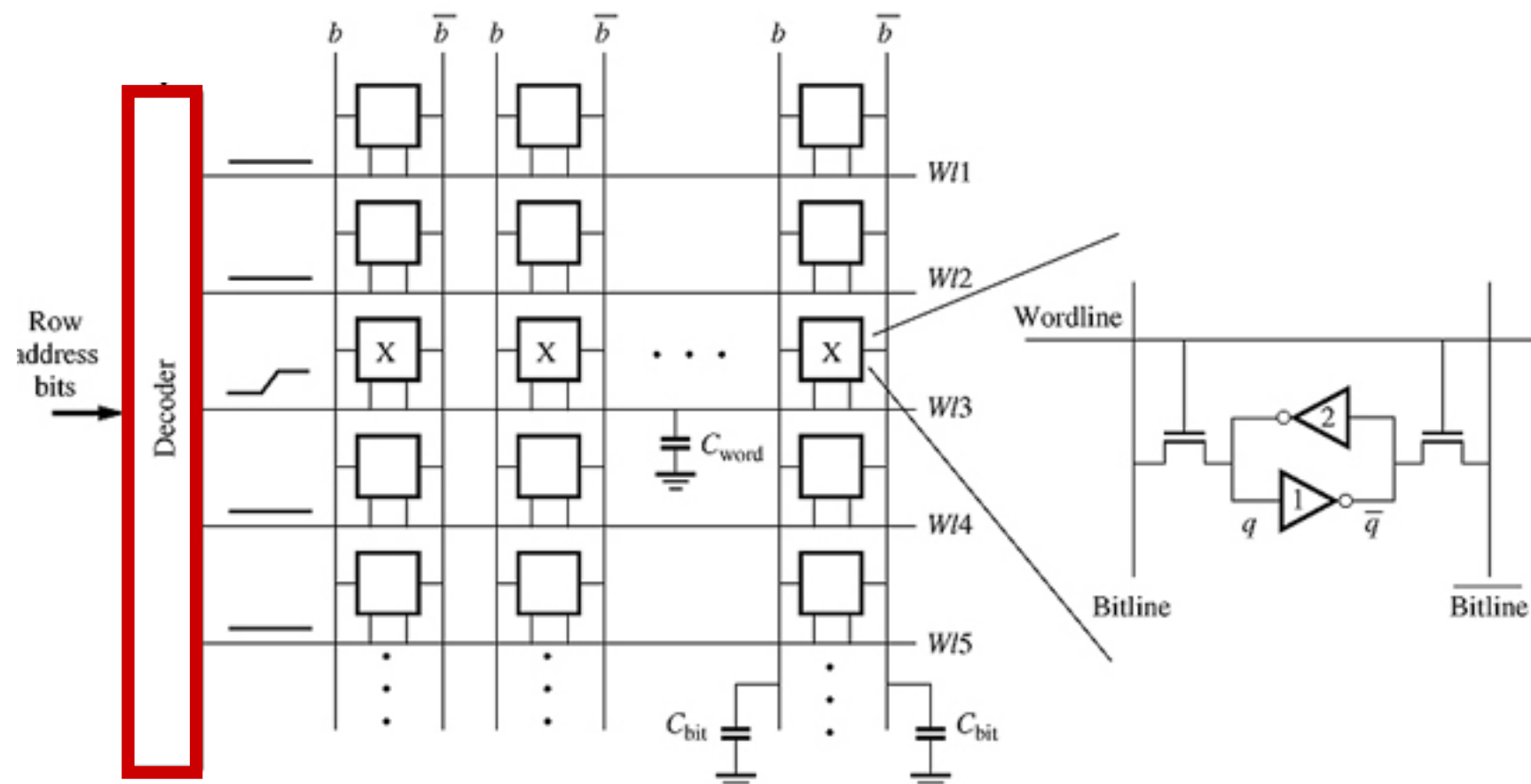- Look at decoder for 256x256 memory block (8KBytes)




Possible Decoder

 - 256 8-input AND gates
 - Each built out of a tree of NAND gates and inverters
- Need to drive a lot of capacitance (SRAM cells)
 - What's the best way to do this?




Possible AND8

 - Build 8-input NAND gate using 2-input gates and inverters
- Is this the best we can do?
- Is this better than using fewer NAND4 gates?



 Problem Setup

- Goal: Build fastest possible decoder with static CMOS logic
- What we know
 - Basically need 256 AND gates, each one of them drives one word line



Problem Setup (1)

- Each wordline has 256 cells connected to it
- $C_{WL} = 256 * C_{cell} + C_{wire}$
 - Ignore wire for now
- Assume that decoder input capacitance is $C_{address} = 4 * C_{cell}$

Problem Setup (2)


- Each address bit drives $2^8/2$ AND gates
 - A0 drives $1/2$ of the gates, A0_b the other $1/2$ of the gates
- Total fanout on each address wire is:

$$F = \Pi B \frac{C_{load}}{C_{in}} = 128 \frac{(256 C_{cell})}{4 C_{cell}} = 2^7 \frac{(2^8 C_{cell})}{2^2 C_{cell}} = 2^{13}$$

Decoder Fan-Out

- F of 2^{13} means that we will want to use more than $\log_4(2^{13}) = 6.5$ stages to implement the AND8
- Need many stages anyways
 - So what is the best way to implement the AND gate?
 - Will see next that it's the one with the most stages and least complicated gates

8-Input AND

 

$$LE : 9/2 \quad 1$$

$$\Pi LE = 9/2$$

$$P = 8 + 1$$

$$LE : 5/2 \quad 3/2$$

$$\Pi LE = 15/4$$

$$P = 4 + 2$$


$$LE : 3/2 \quad 3/2 \quad 3/2 \quad 1$$

$$\Pi LE = 27/8$$

$$P = 2 + 2 + 2 + 1$$


8-Input AND

 - Using 2-input NAND gates
 - 8-input gate takes 6 stages
- Total LE is $(3/2)^3 \approx 3.4$
- So PE is $3.4 * 2^{13}$ – optimal N of ~ 7.4







Decoder So Far

 - 256 8-input AND gates
 - Each built out of tree of NAND gates and inverters
- Issue:
 - Every address line has to drive 128 gates (and wire) right away
 - Forces us to add buffers just to drive address inputs




Look Inside Each AND8 Gate

    

Predecoders


- Use a single gate for each of the shared terms
 - E.g., from A_0 , $\overline{A_0}$, A_1 , and $\overline{A_1}$, generate four signals: A_0A_1 , $\overline{A_0}A_1$, $A_0\overline{A_1}$, $\overline{A_0}\overline{A_1}$
- In other words, we are decoding smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding

Predecoder and Decoder

 

Predecode Options

 - Larger predecode usually better:
- More stages before the long wires
 - Decreases their effect on the circuit
- Fewer number of long wires switches
 - Lower power
- Easier to fit 2-input gate into cell pitch




Administrivia

- Projects
 - Checkpoints 2 are this Friday
- Homework 9 due in a week



Building Larger Arrays

Building Larger Custom Arrays

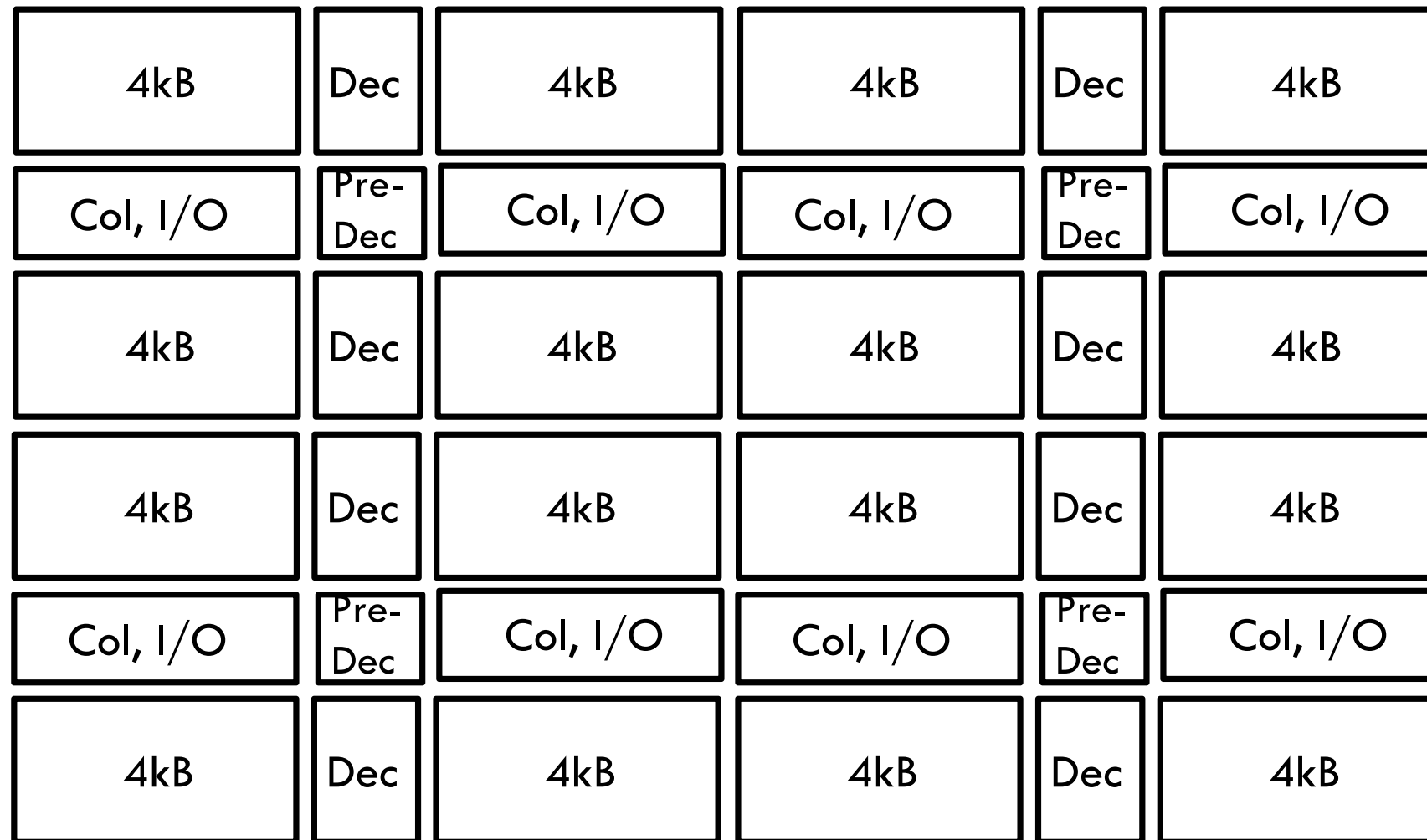


- Each subarray is 2-8kB
- Hierarchical decoding
- Peripheral overhead is 30-50%
- Delay is wire dominated
- Scratchpads, caches, TLBs

Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

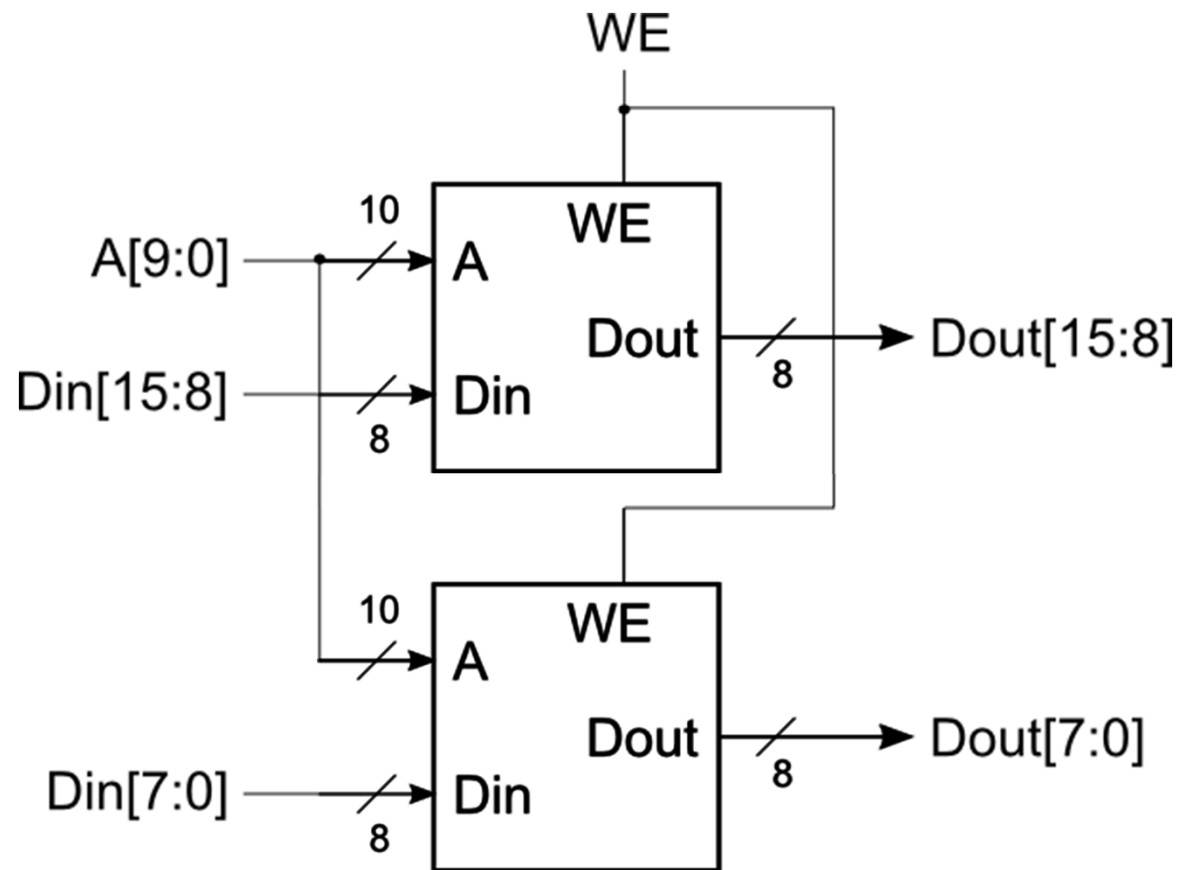Increasing the width. Example: given 1Kx8, want 1Kx16



Cascading Memory-Blocks

How to make larger memory blocks out of smaller ones.

Increasing the depth. Example: given 1Kx8, want 2Kx8


The diagram illustrates the cascading of two 1Kx8 memory blocks to create a 2Kx8 memory block. Each block has a 10-bit address (A[9:0]), an 8-bit data input (Din), an 8-bit data output (Dout), and a write enable (WE) signal. The address A[10] is used as a select input for a 2-to-1 multiplexer. The multiplexer's inputs are the Douts of the two memory blocks. The output of the multiplexer is the final 8-bit data output, Dout[7:0].

EECS151/251A L19 CACHES

29

How to make larger memory blocks out of smaller ones.

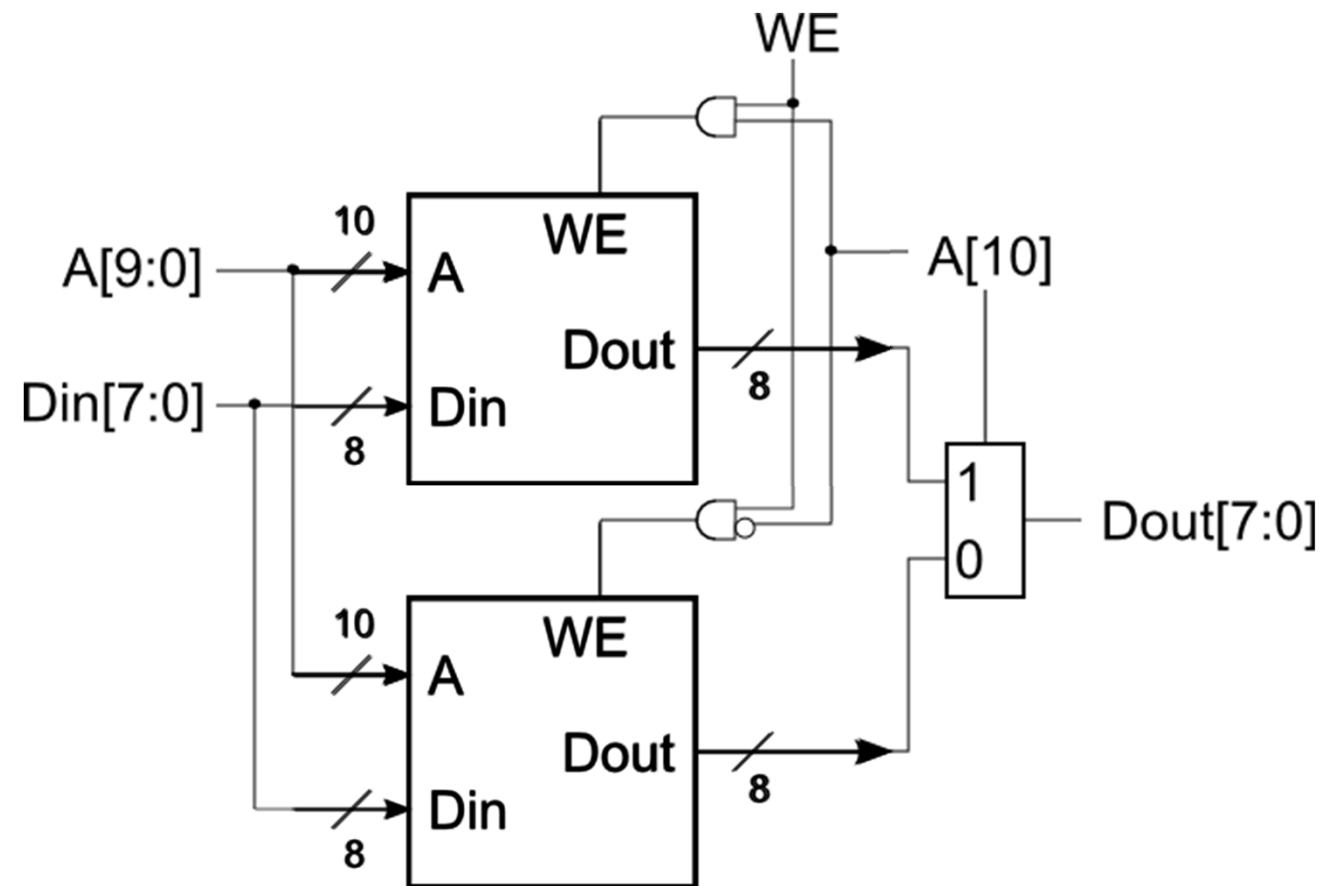
Increasing the depth. Example: given 1Kx8, want 2Kx8



Adding Ports to Primitive Memory Blocks

Adding a read port to a simple dual port (SDP) memory.

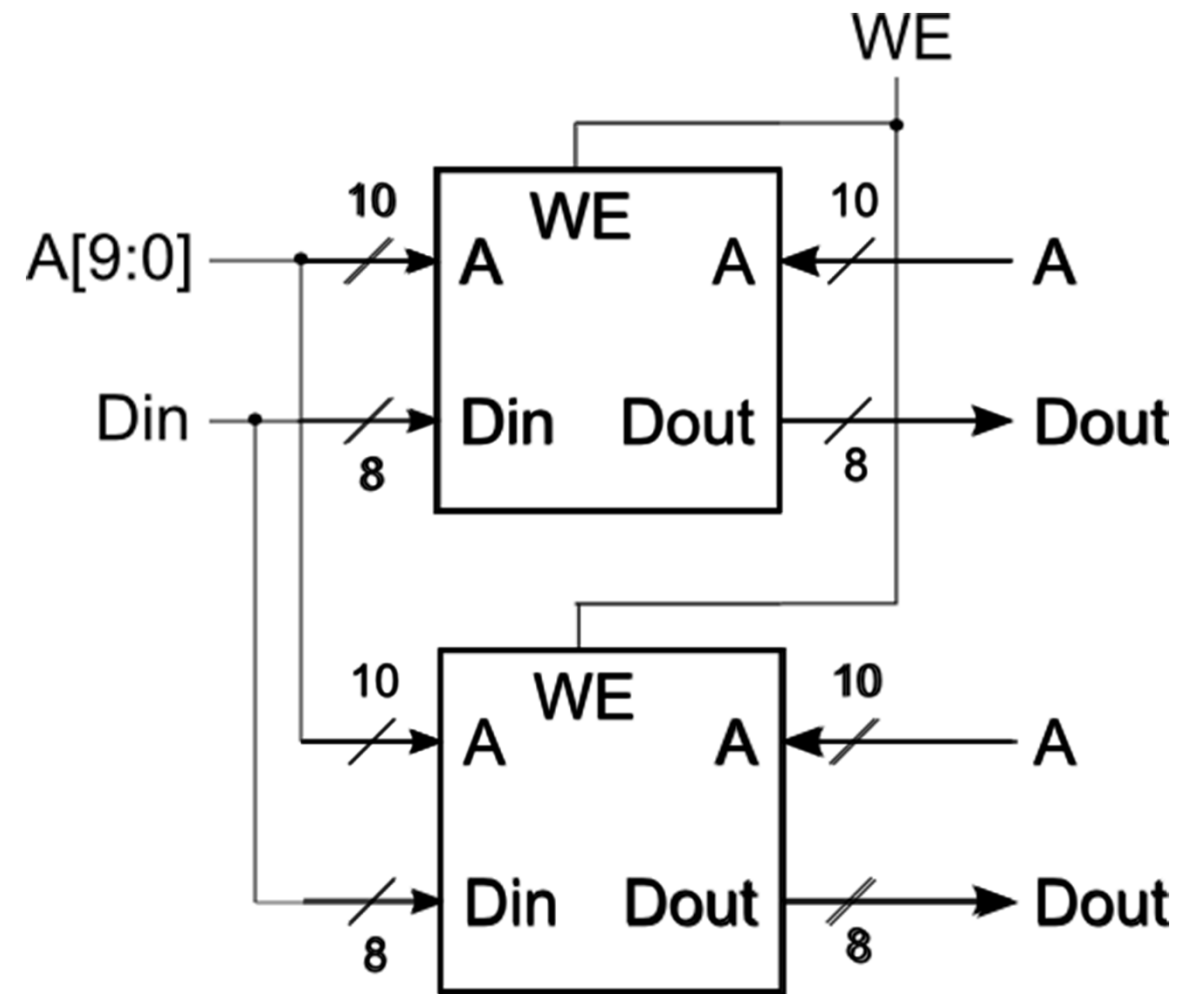
Example: given 1Kx8 SDP, want 1 write & 2 read ports.



Adding Ports to Primitive Memory Blocks

How to add a write port to a simple dual port memory.

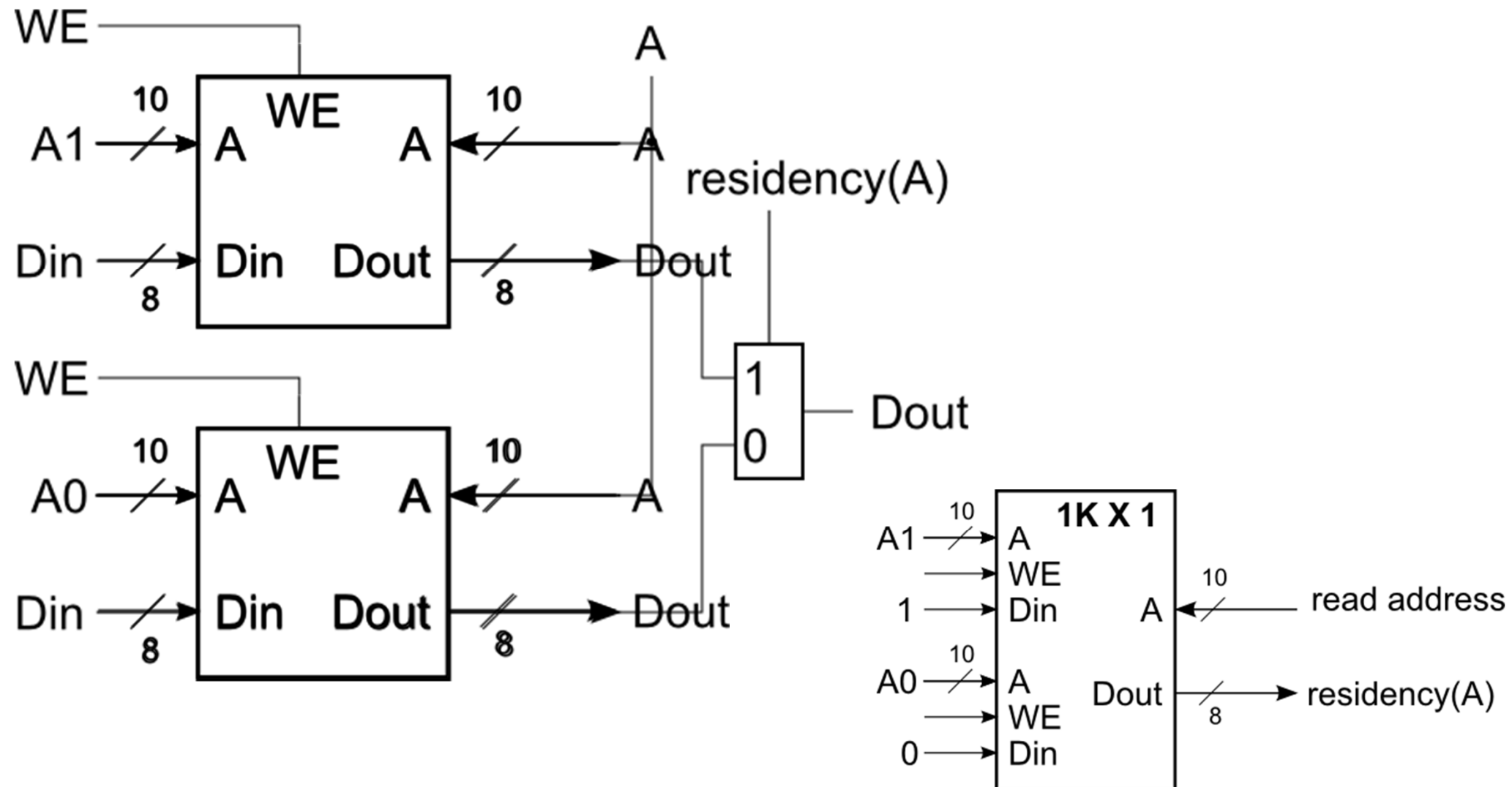Example: given 1Kx8 SDP, want 1 read & 2 write ports.





Caches

Caches (Review from 61C)

- **Two Different Types of Locality:**
 - **Temporal locality (Locality in time):** If an item is referenced, it tends to be referenced again soon.
 - **Spatial locality (Locality in space):** If an item is referenced, items whose addresses are close by tend to be referenced soon.
- **By taking advantage of the principle of locality:**
 - **Present the user with as much memory as is available in the cheapest technology.**
 - **Provide access at the speed offered by the fastest technology.**
- **DRAM is slow but cheap and dense:**
 - **Good choice for presenting the user with a BIG memory system**
- **SRAM is fast but expensive and not as dense:**
 - **Good choice for providing the user FAST access time.**

Example: 1 KB Direct Mapped Cache with 32 B Blocks

For a 2^N -byte cache:

- The uppermost $(32 - N)$ bits are always the **Cache Tag**
- The lowest M bits are the **byte-select offset** (**Block Size** = 2^M)

Diagram illustrating the structure of a 1 KB Direct Mapped Cache with 32 B Blocks.

The **Block address** (32 bits) is divided into three fields:

- Cache Tag** (28 bits, bits 31 to 4): Example: 0x50. This field is stored as part of the cache "state".
- Cache Index** (4 bits, bits 3 to 0): Example: 0x01. This field selects the cache entry.
- Offset** (0 bits, bit 0): Example: 0x00. This field selects the byte within the cache entry.


The cache structure consists of 16 entries (rows). Each entry contains:

- Valid Bit**: A single bit indicating if the entry is valid.
- Cache Tag**: 28 bits, matching the upper 28 bits of the block address.
- Cache Data**: 32 bytes (256 bits), divided into four 8-byte segments (Byte 31 to Byte 0, Byte 63 to Byte 32, etc.).

The **Cache Index** (0x01) selects the second entry (index 1). The **Offset** (0x00) selects the first byte (Byte 0) of the Cache Data in that entry.

For a 2^N -byte cache:

 - The uppermost (32 - N) bits are always the Cache Tag
- The lowest M bits are the byte-select offset (Block Size = 2^M)




Fully Associative Cache

Fully Associative Cache

- Ignore cache Index for now
- Compare the Cache Tags of all cache entries in parallel (expensive...)_
- Example: Block Size = 32 B blocks, we need N 27-bit comparators

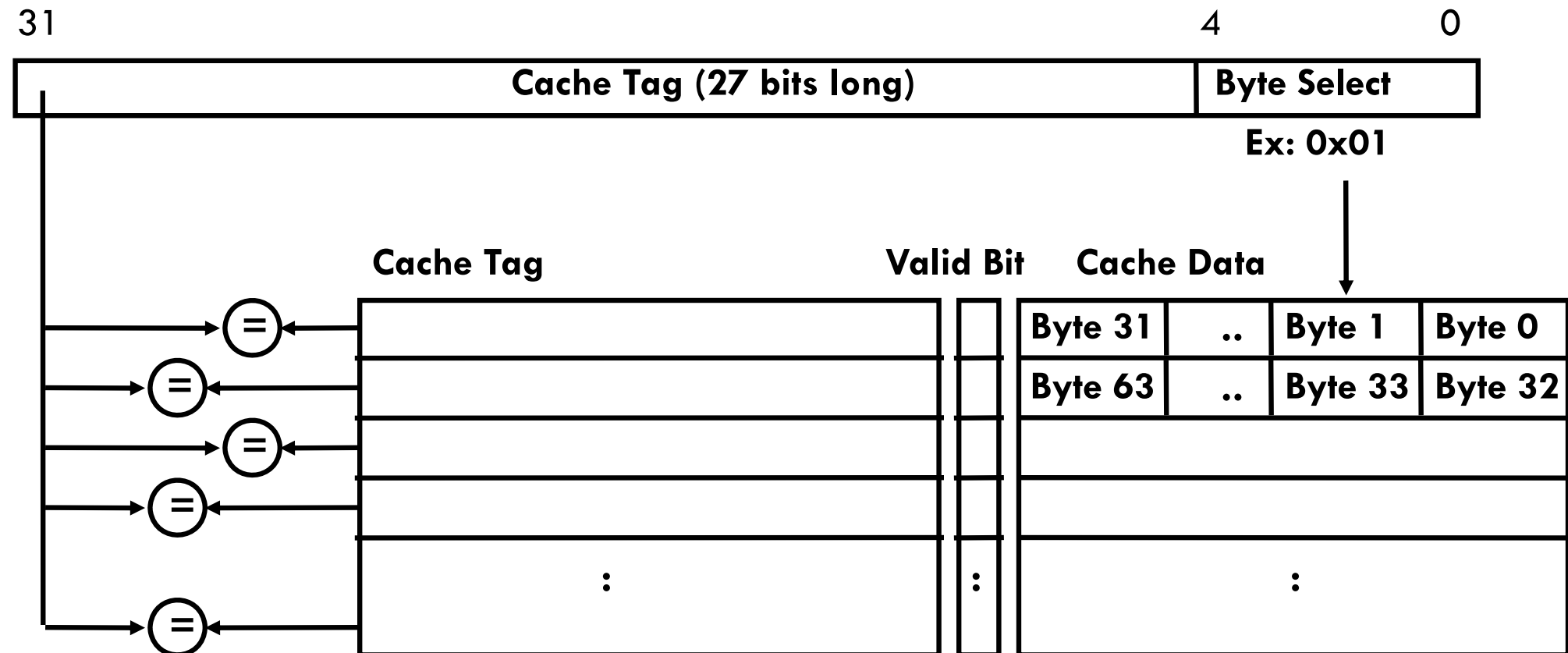By definition: Conflict Miss = 0 for a fully associative cache




Set Associative Cache

N-way set associative: N entries for each Cache Index

- N direct mapped caches operates in parallel

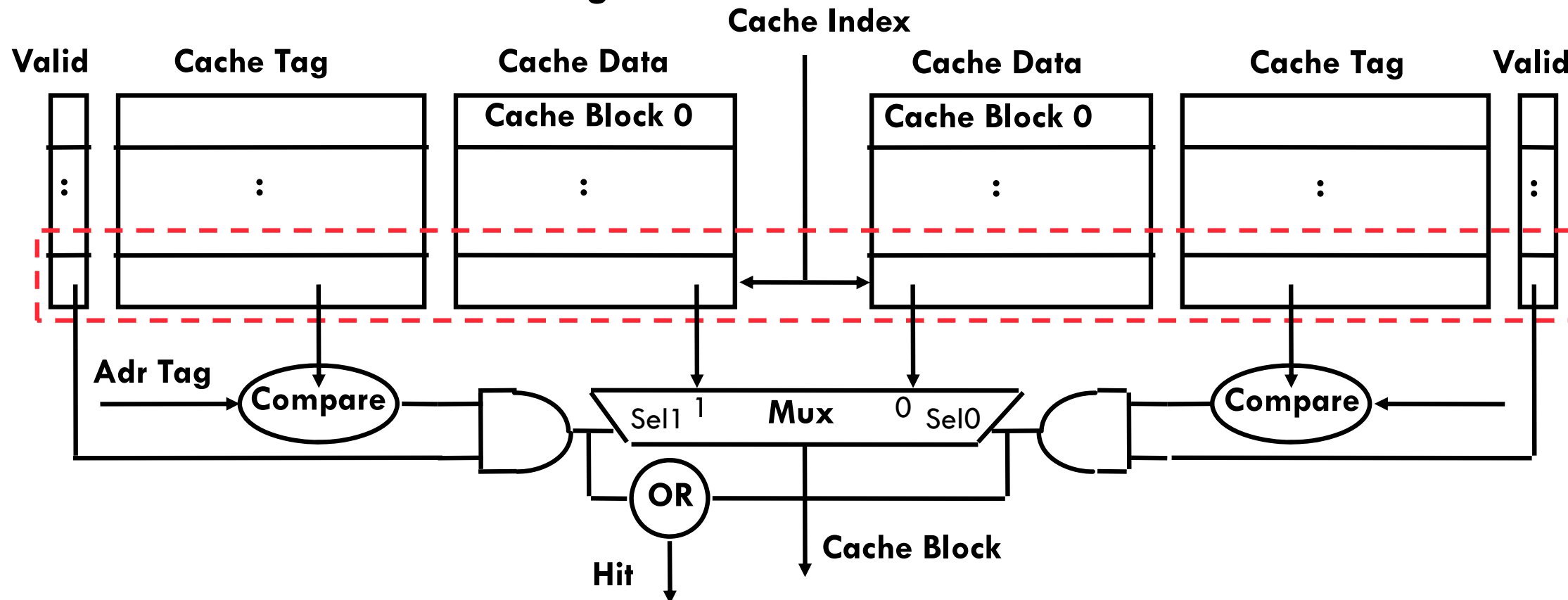Example: Two-way set associative cache

- Cache Index selects a “set” from the cache
- The two tags in the set are compared to the input in parallel
- Data is selected based on the tag result




Disadvantage of Set Associative Cache

N-way Set Associative Cache versus Direct Mapped Cache:

- N comparators vs. 1
- Extra MUX delay for the data
- Data comes **AFTER** Hit/Miss decision and set selection

In a direct mapped cache, Cache Block is available **BEFORE** Hit/Miss:

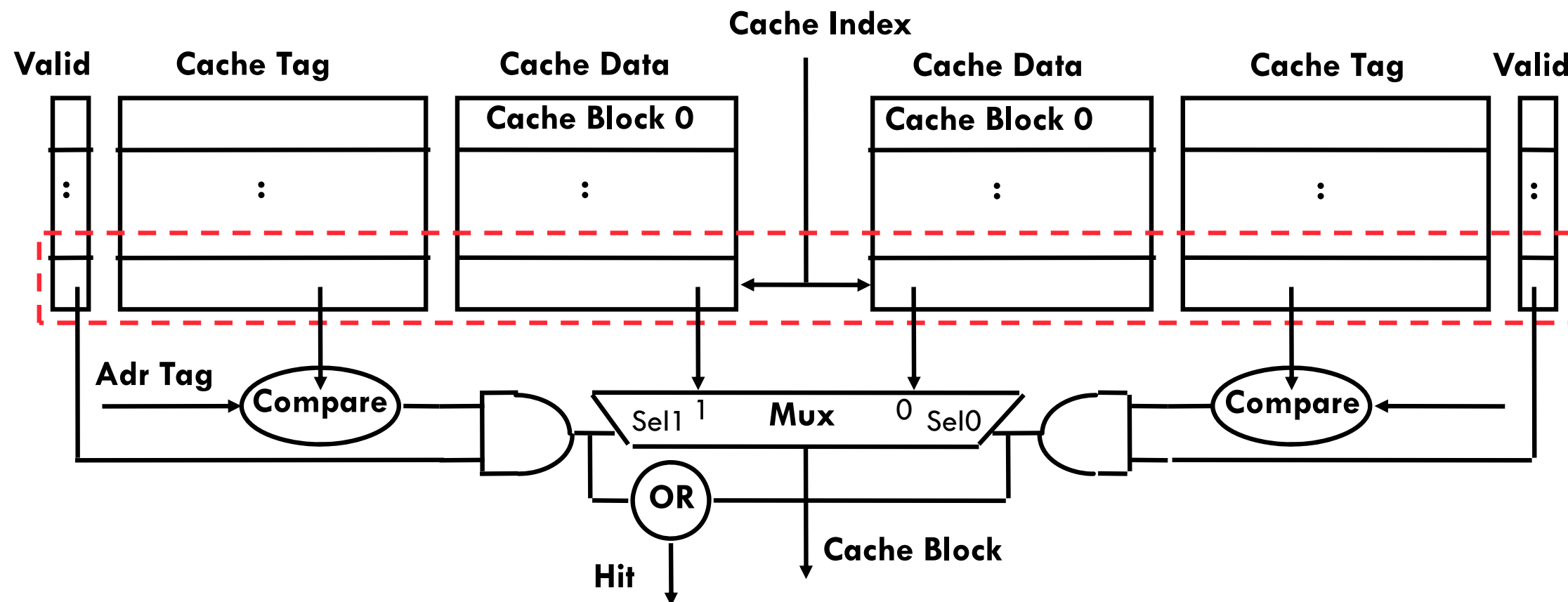- Possible to assume a hit and continue. Recover later if miss.



Block Replacement Policy

- Direct-Mapped Cache
 - index completely specifies position which position a block can go in on a miss
- N-Way Set Assoc
 - index specifies a set, but block can occupy any position within the set on a miss
- Fully Associative
 - block can be written into any position
- Question: if we have the choice, where should we write an incoming block?
 - If there's a valid bit off, write new block into first invalid.
 - If all are valid, pick a replacement policy
 - rule for which block gets “cached out” on a miss.

Block Replacement Policy: LRU

- LRU (Least Recently Used)
 - Idea: cache out block which has been accessed (read or write) least recently
 - Pro: **temporal locality** → recent past use implies likely future use: in fact, this is a very effective policy
 - Con: with 2-way set assoc, easy to keep track (one LRU bit); with 4-way or greater, requires more complicated hardware and more time to keep track of this

Summary

- SRAM and regfile cells can have multiple R/W ports
- Memory decoding is done hierarchically
 - Wire-limited in large arrays
- Multiple cache levels make memory appear both fast and big
- Direct mapped and set-associative cache