

# EECS151 : Introduction to Digital Design and ICs


## Lecture 15 – Adders

**Bora Nikolić and Sophia Shao**


 
### Infineon Flies Under the Radar on Google's Soli

Google last week rolled out its Pixel 4 smartphone, whose claim to fame is a radar-based technology that makes it the first smartphone featuring “Motion Sense” capabilities.



EE Times, 10/21/2019



# Delay Optimization

- Wires contributes to delay and energy, especially in modern technology.
- We can use RC models to capture wire delay.
- Energy becomes an increasingly important optimization goal.
  - Dynamic Energy
  - Static Energy




# Binary Adders
 
# Binary Adder

- Adders

```
module add32(i0,i1,sum);  
input [31:0] i0,i1;  
output [31:0] sum;  
  
assign sum = i0 + i1;  
endmodule
```




What's inside?

Depends on:

- Performance/power requirements
- Number of bits

# Single-Bit Full-Adder

 


A	B	C <sub>in</sub>	S	C <sub>o</sub>	Carry Status
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Carry status = {generate, propagate, delete}

# Single-Bit Full Adder

- Logic equations

 


$$S = A \oplus B \oplus C_i$$

$$S = A \bar{B} \bar{C}_i + \bar{A} B \bar{C}_i + \bar{A} \bar{B} C_i + A B C_i$$

$$C_o = A B + B C_i + A C_i$$

# Static CMOS Full Adder

- Direct mapping of logic equations

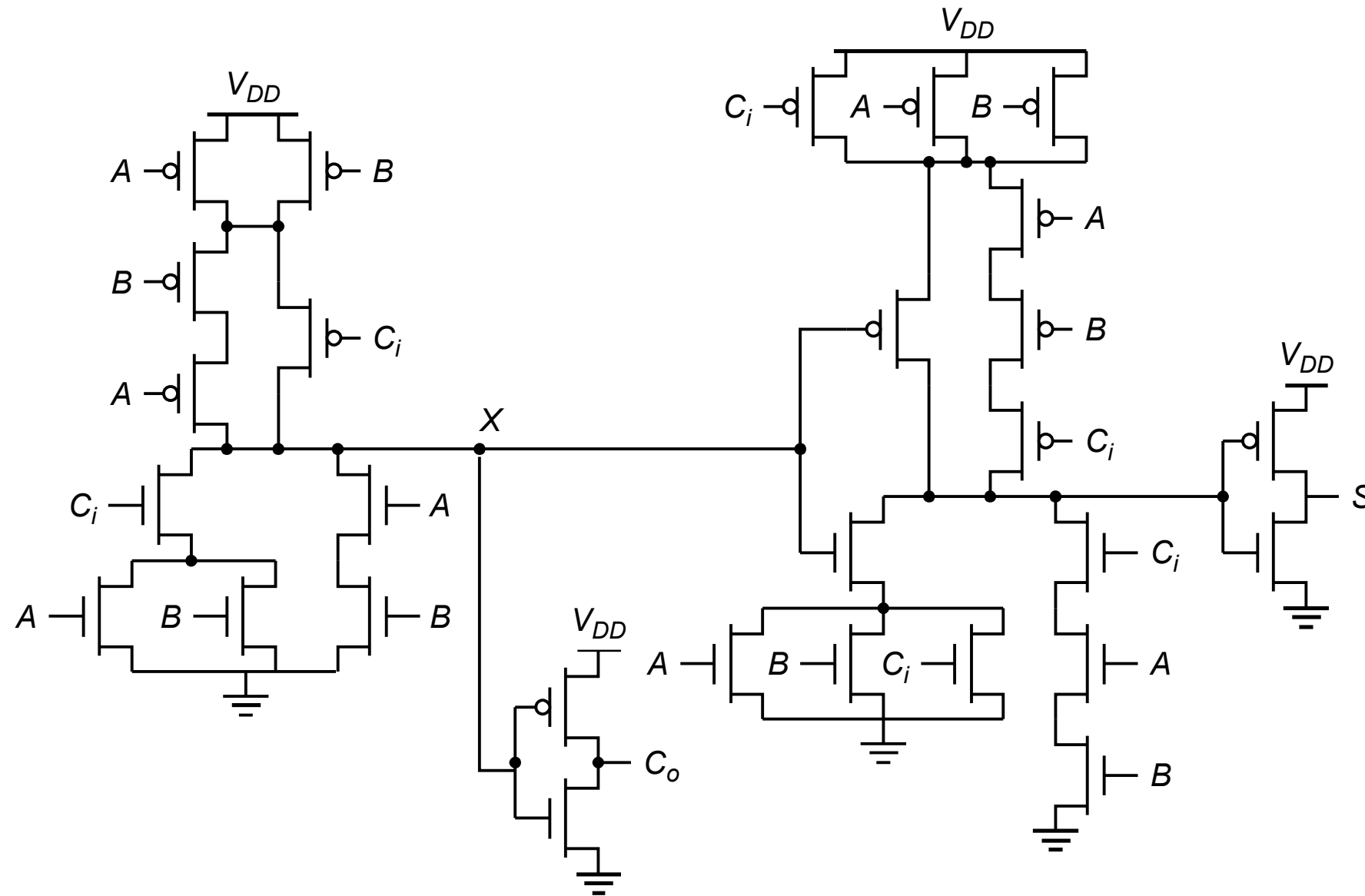

28 Transistors

# Express Sum and Carry as a function of P, G, D

- Define generate, propagate and delete as functions of A, B
  - Will use two at a time

**Generate (G) = AB**

**Propagate (P) = A + B (= A  $\oplus$  B)**

**Delete =  $\overline{A} \overline{B}$**

$$C_o = A B + B C_i + A C_i = G + P C_i$$


A	B	C <sub>i</sub>	S	C <sub>o</sub>	P	G
0	0	0	0	0	0	0
0	0	1	1	0	1	0
0	1	0	1	0	1	0
0	1	1	0	1	x	1
1	0	0	1	0	0	0
1	0	1	0	1	1	0
1	1	0	0	1	1	0
1	1	1	1	1	X	1

Can also derive expressions for C<sub>o</sub> based on D and P



# The Ripple-Carry Adder

- 4-bit adder

 


**Worst case delay linear with the number of bits**

$$t_d = O(N)$$

$$t_{\text{adder}} = (N-1)t_{\text{carry}} + t_{\text{sum}}$$

**Goal: Make the fastest possible carry path circuit**


# Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$
 
# Minimize Critical Path by Reducing Inverting Stages




**Exploit Inversion Property**

# A Better Structure: The Mirror Adder

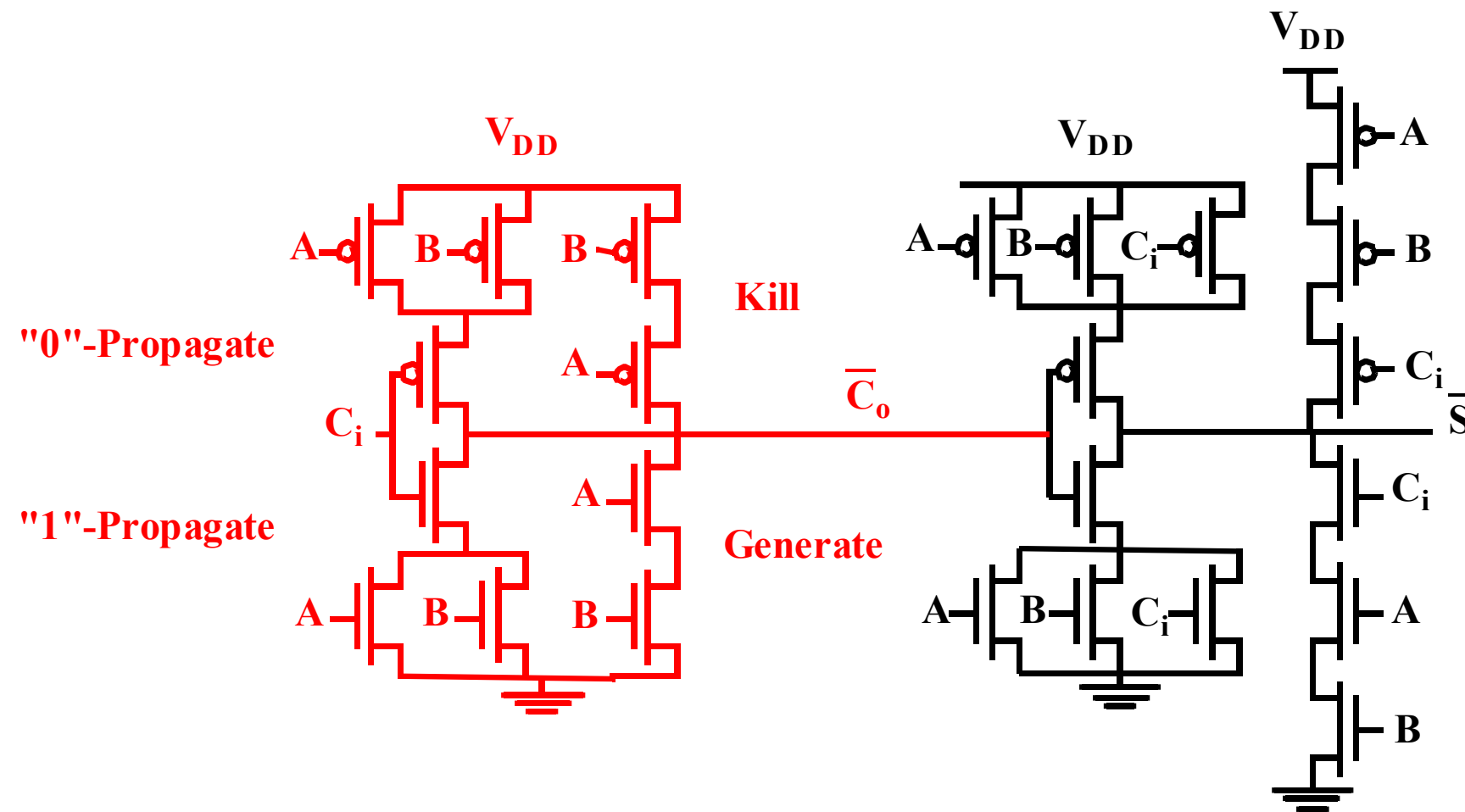

24 transistors

# Sizing the Mirror Adder

 

- $C_{\text{load}} = C_{C_i} + x = 2C_{C_i}$


$\rightarrow C_{C_i} =$

- Reduce size of G and K stacks to reduce diffusion loading



# The Mirror Adder

- The NMOS and PMOS chains are **completely symmetrical**.  
A maximum of two series transistors in the carry-generation stack.
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be smaller.
- The transistors connected to  $C_i$  are placed closest to the output.
- Minimize the the capacitance at node  $C_o$ .

# Transmission Gate Full Adder

 

Setup

  

Sum Generation

Carry Generation




# Carry Bypass Adders




# Carry-Bypass Adder

- Also called 'carry skip'

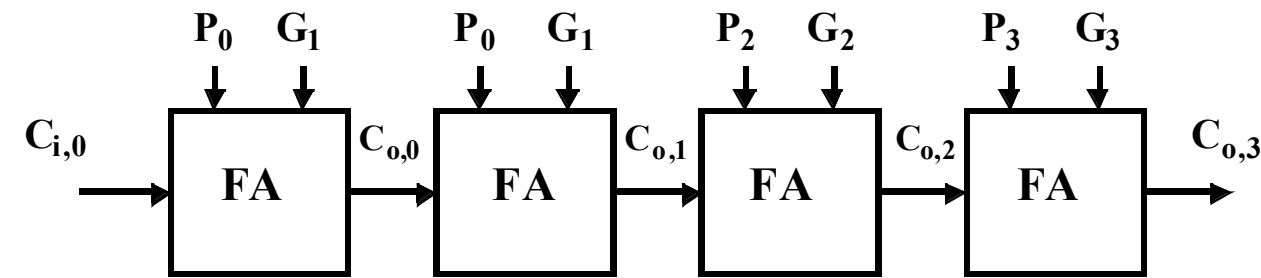


Also called  
Carry-Skip

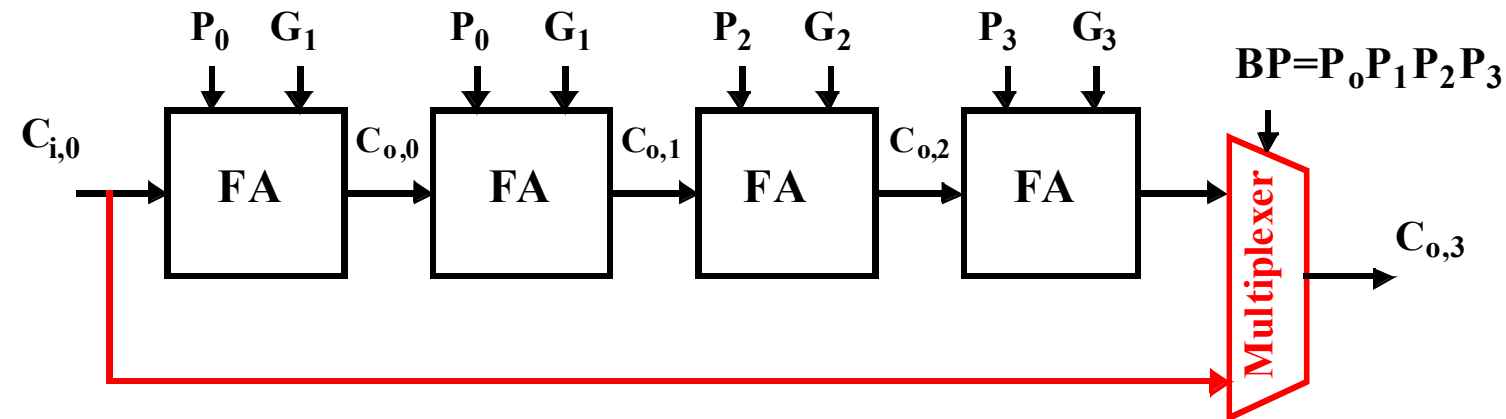


Idea: If ( $P_0$  and  $P_1$  and  $P_2$  and  $P_3 = 1$ )  
then  $C_{03} = C_0$ , else "kill" or "generate".

## Carry-Bypass Adder (cont.)

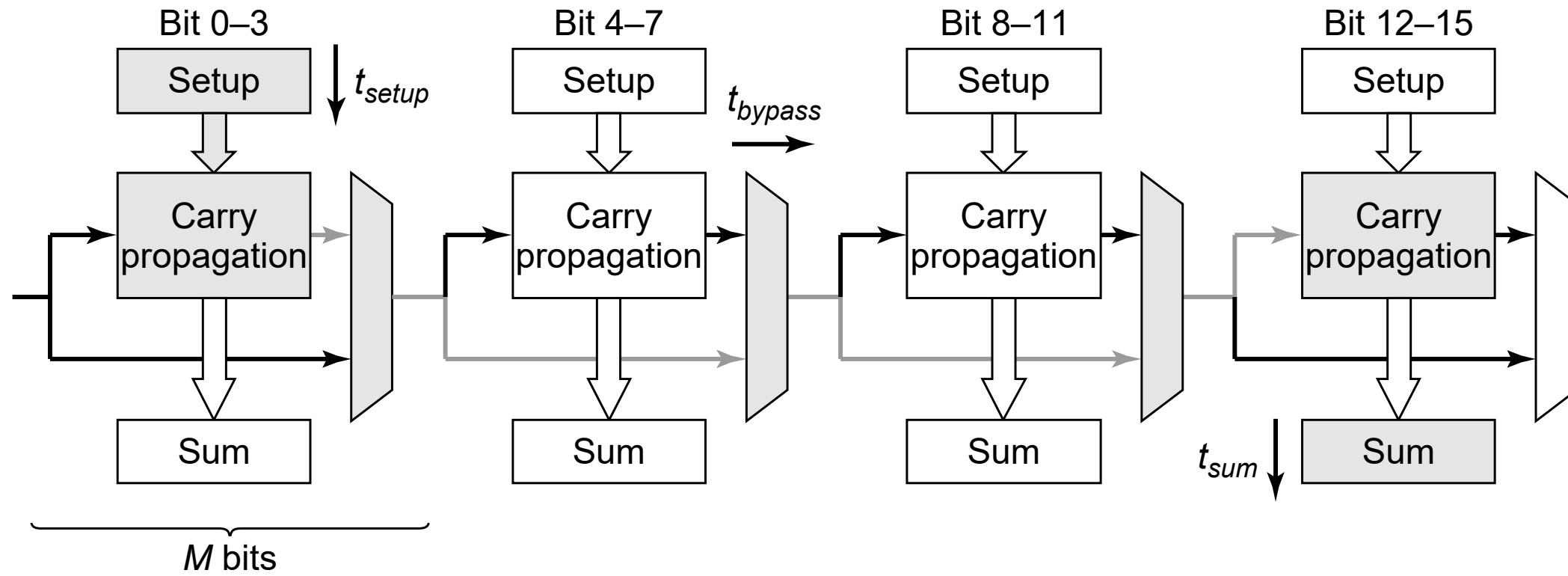


$$t_{\text{adder}} = t_{\text{setup}} + M t_{\text{carry}} + (N/M - 1) t_{\text{bypass}} + (M - 1) t_{\text{carry}} + t_{\text{sum}}$$

# Carry Ripple versus Carry Bypass

 

- Depends on technology, design constraints

# To Design a Faster Carry-Bypass Adder

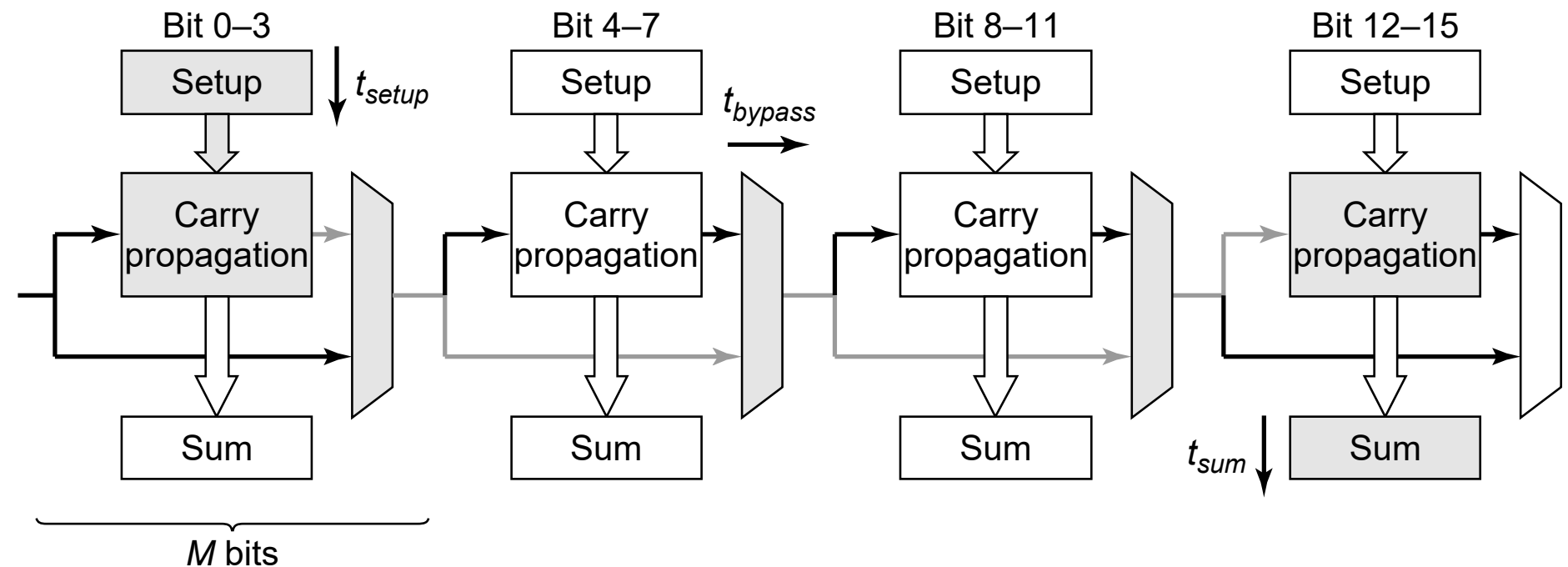


- a) uniform groups of 4 are optimal
- b) uniform groups  $>4$  are optimal
- c) uniform groups  $>4$  are optimal
- d) increasing group size with higher bit position
- e) Wider groups around mid pit positions are optimal




# Carry-Select Adders


# Carry-Select Adder

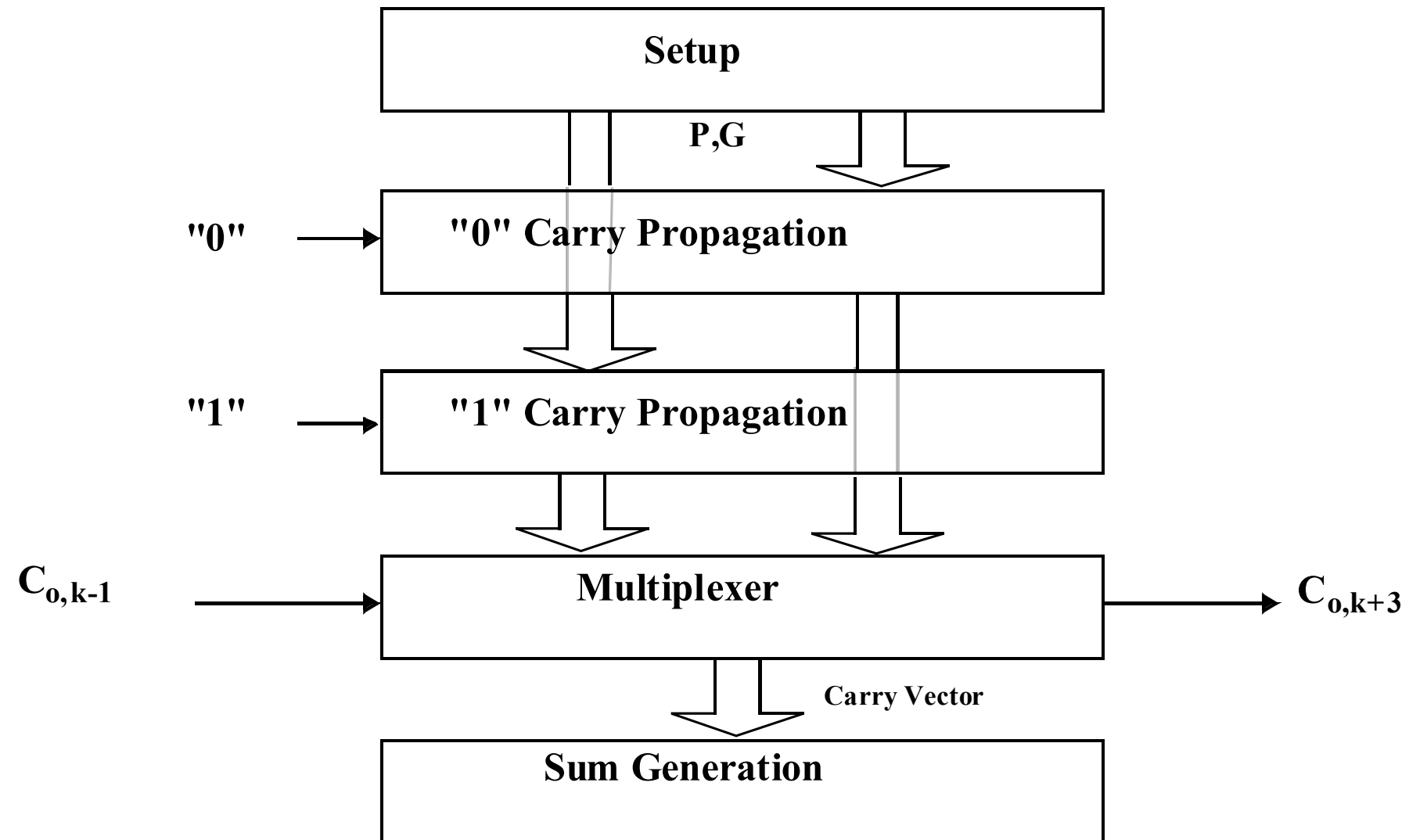

# Carry Select Adder: Critical Path

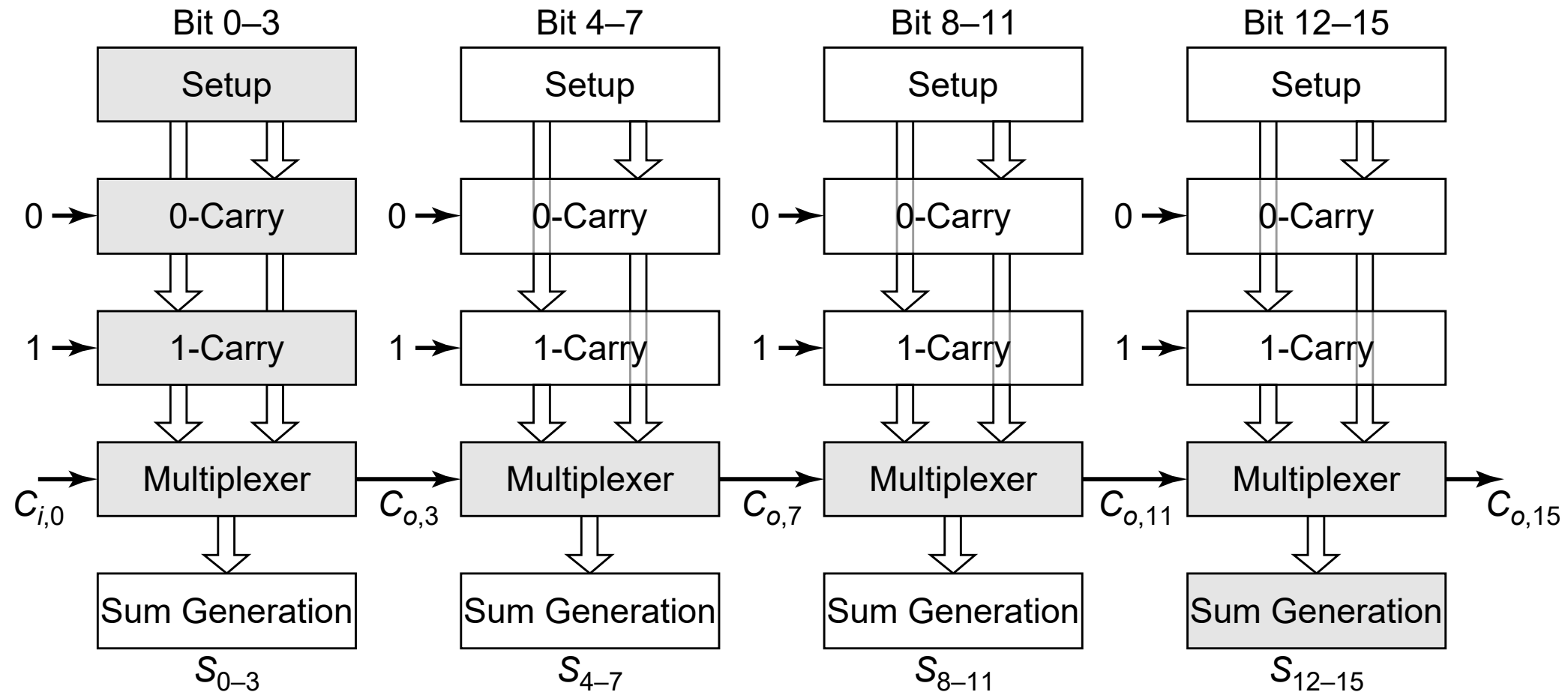


# Linear Carry Select

 

$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$




# Square Root Carry Select

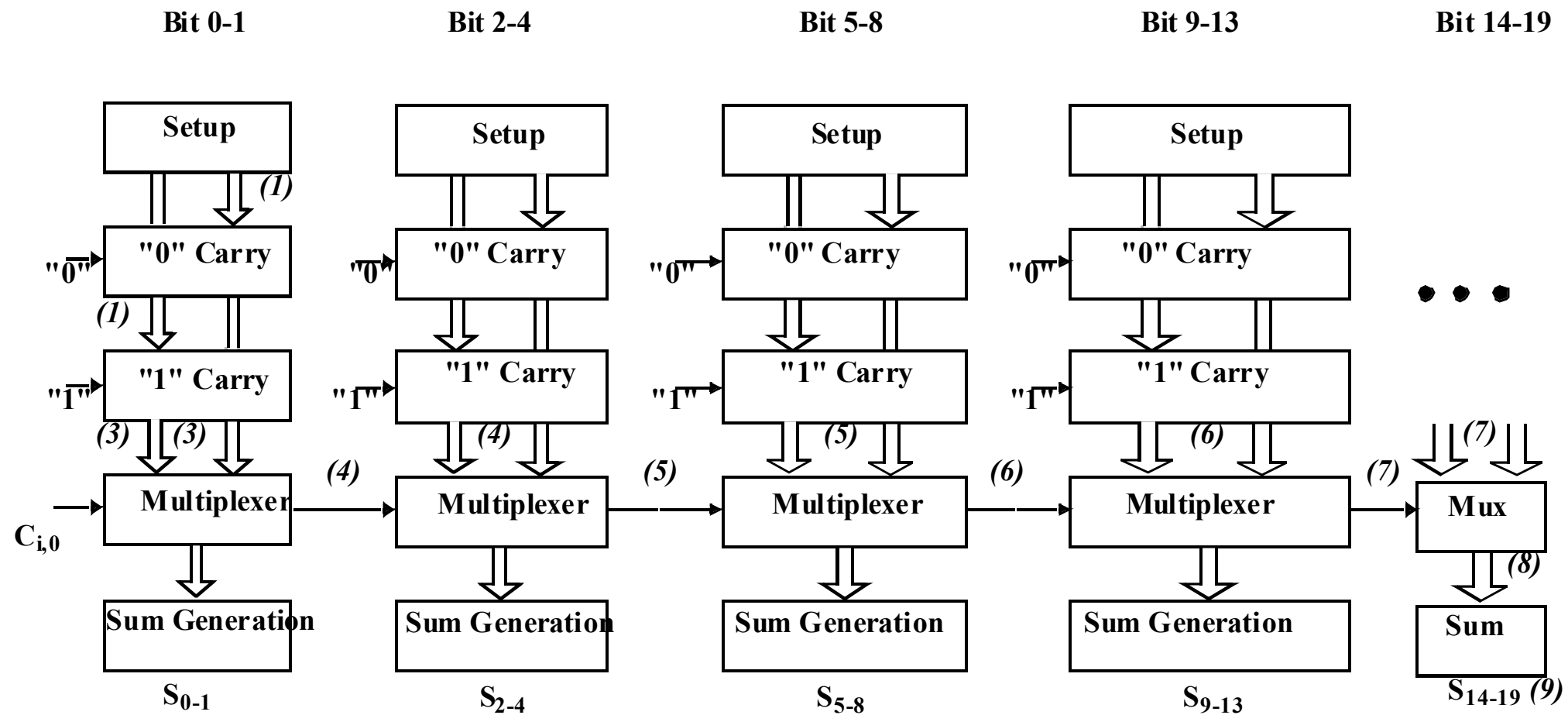

$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$

# Adder Delays - Comparison

 


# Administrivia

- Midterm 2 next week!
  - Covers material up to this Wednesday
- Power outages: We are still trying to keep lectures, homework, projects in sync
  - Please talk to us if you feel overwhelmed



# Carry-Lookahead Adders

# Lookahead - Basic Idea

 

$$C_{o,k} = f(A_k, B_k, C_{o,k-1}) = G_k + P_k C_{o,k-1}$$

# Lookahead: Topology

Expanding lookahead equations:

$$C_{o,1} = G_1 + P_1 C_{i,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

Carry at bit k:


$$C_{o,k} = G_k + P_k (G_{k-1} + P_{k-1} C_{o,k-2})$$

Expanding at bit k:

$$C_{o,k} = G_k + P_k (G_{k-1} + P_{k-1} (\dots + P_1 (G_0 + P_0 C_{i,0}) \dots))$$

Carry-lookahead gate grows at each bit position!
 
$$C_o = A B + B C_i + A C_i = G + P C_i$$



# Carry Lookahead Trees

Build the carrylookahead tree as a hierarchy of gates

$$C_{o,0} = G_0 + P_0 C_{i,0}$$

$$C_{o,1} = G_1 + P_1 C_{i,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$\begin{aligned} C_{o,2} &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0} \\ &= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{O,0} \end{aligned}$$

Can continue building the tree hierarchically.

# Logarithmic (Tree) Adders – Idea


- “Look ahead” across groups of multiple bits to figure out the carry

- Example with two bit groups:

$$P_{1:0} = P_1 \cdot P_0, G_{1:0} = G_1 + P_1 \cdot G_0, \rightarrow C_{out1} = G_{1:0} + P_{1:0} \cdot C_{0,in}$$

- Combine these groups in a tree structure:


- Delay is now  
 $\sim \log_2(N)$

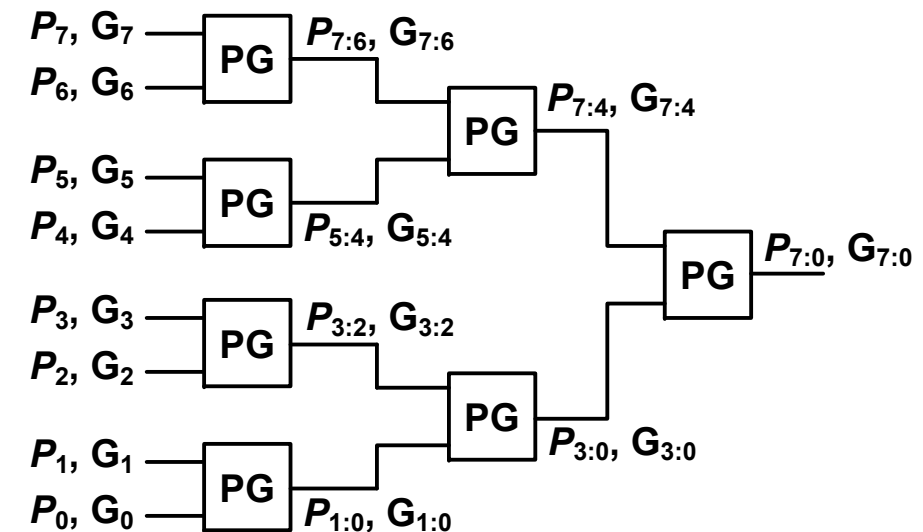


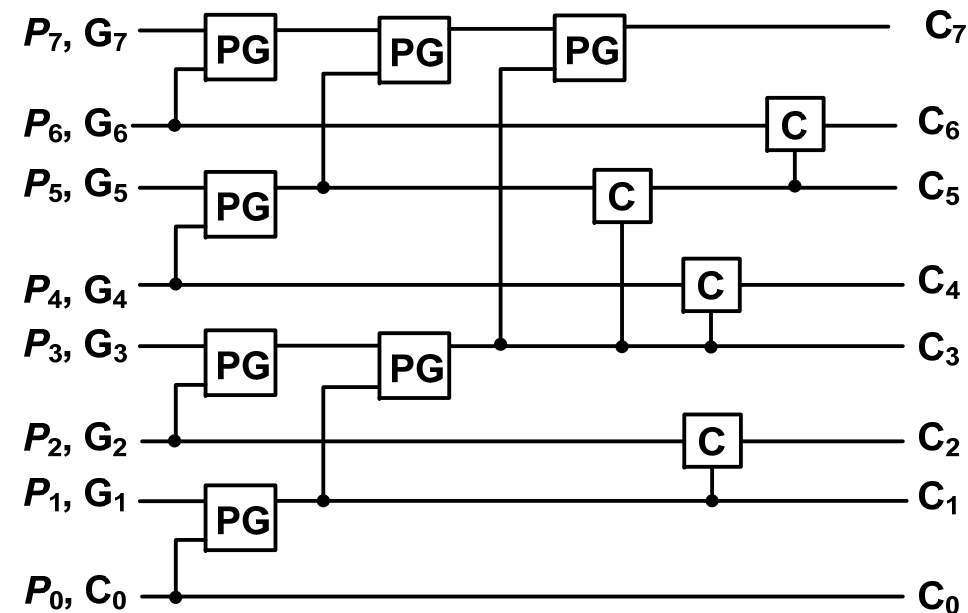
# Rest of the Tree


- Previous picture shows only half of the algorithm
  - Need to generate carries at individual bit positions too



# Many Kinds of Tree Adders


- ❑ Many ways to construct these tree (or “carry lookahead”) adders
  - Many of these variations named after the people who first came up with them
- ❑ Most of these vary three basic parameters:
  - Radix: how many bits are combined in each PG gate
    - Previous example was radix 2; often go up to radix 4
  - Tree depth: stages of logic to the final carry. Must be at least  $\log_{\text{Radix}}(N)$
  - Sparseness

# Tree Adders

 


**16-bit radix-2 Kogge-Stone tree**

# Tree Adders

 


**16-bit radix-4 Kogge-Stone Tree**

# Sparse Trees

 

**16-bit radix-2 sparse tree with sparseness of 2**

# Tree Adders

 

**Brent-Kung Tree**

# Summary

- Binary adders are a common building block of digital systems
- Carry is in the critical path
- Carry-bypass, carry-select are usually faster than ripple-carry for lengths  $> 8$
- Carry-lookahead,  $O(\sim \log N)$  is often the fastest adder with  $N > 16$