

EECS151 : Introduction to Digital Design and ICs

Lecture 12 – Delays


Bora Nikolić and Sophia Shao



OpenAI's AI-powered robot learned how to solve a Rubik's cube one-handed

Oct. 15, 2019, Artificial intelligence research organization OpenAI has achieved a new milestone in its quest to build general purpose, self-learning robots. The group's robotics division says Dactyl, its humanoid robotic hand first developed last year, has learned to solve a Rubik's cube one-handed.

The Verge, Oct. 15, 2019.

 

OpenAI Nikolić, Shao Fall 2019 © UCB

Review


- Modern lithography is reflected in design rules
- FinFET widths are quantized
- MOS transistors can be modeled as resistive switches
 - They also have a capacitance




MOS Transistor as a Switch

MOS Transistor as a Resistive Switch

MOS Transistor

 


A Switch!

 


- V_{GS} controls the switch
 - (it also charges the channel capacitor)

ON/OFF Switch Model of MOS Transistor

 


A More Realistic Model

 


- It is a dimmer!

A Logic Perspective

NMOS Transistor

 


PMOS Transistor

 


AND and OR

- AND

 

$$F = AB$$
$$(F = AB + \overline{A} \cdot 0)$$

- OR

 


$$F = A+B$$
$$(F = A \cdot 1 + \overline{A}B)$$

- Keep in mind – single NMOS/PMOS transistors are imperfect switches!
 - Turns off when $|V_{GS}| = |V_{Th}|$

Peer Instruction

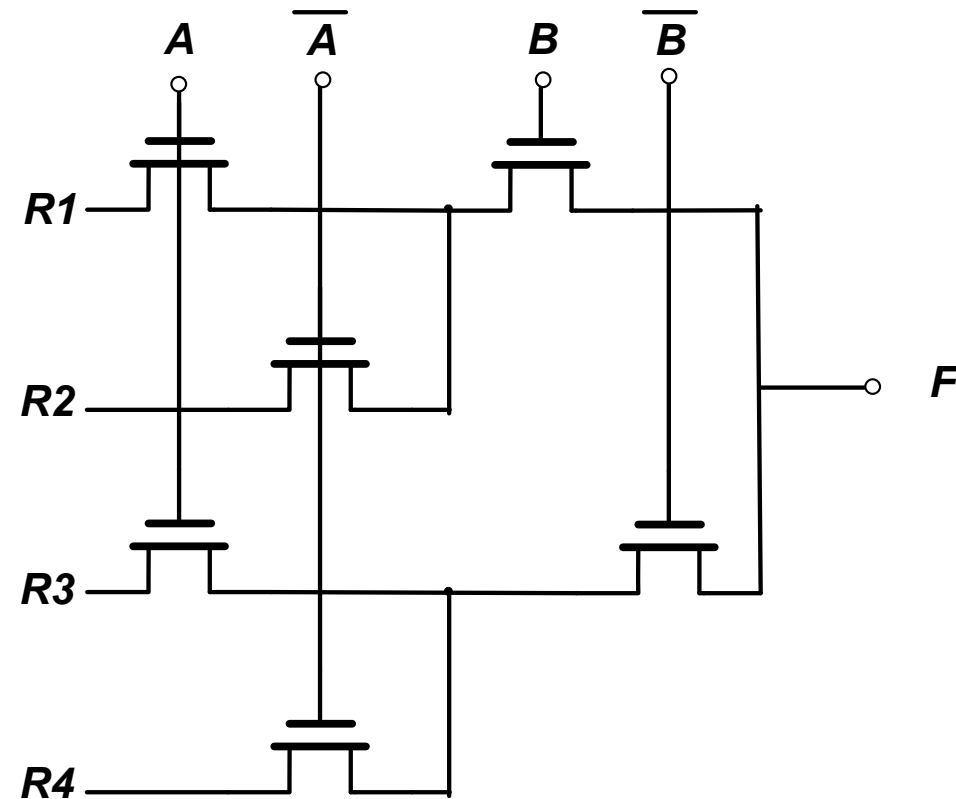- Switch logic
- Which combination of inputs implements $F = AB$?




	R1	R2	R3	R4
a)	1	X	X	X
b)	0	X	X	X
c)	1	0	0	0
d)	1	1	1	0
e)	1	1	1	1
f)	None of the above			




CMOS Inverter

CMOS Inverter

- Simple DC behavior
 - Schematic

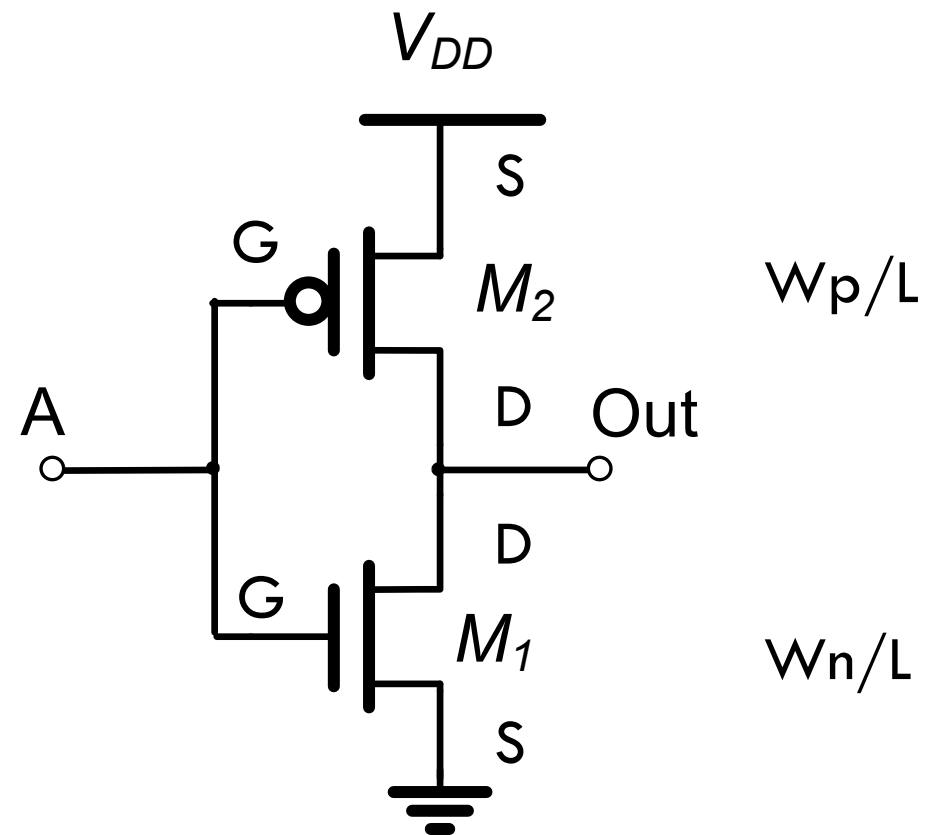


- Switch model

 

$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \end{aligned}$$





Voltage Transfer Characteristic (VTC)

 

$$V_A = V_{DD} + V_{GS,p}$$

$$I_{Dn} = -I_{Dp}$$

$$V_{out} = V_{DD} + V_{DS,p}$$

   
 


$$V_A = V_{GS,n} = V_{DD} - V_{SG,p}$$

$$I_{DS,n} = I_{SD,p}$$

$$V_{Out} = V_{DS,n} = V_{DD} - V_{SD,p}$$

Voltage Transfer Characteristic (VTC)

  

- Can we change switching point (V_A for which $V_{out} = V_{DD}/2$)?

Digital Circuits

- One logic representation

$$\text{Out} = \bar{A}$$

Truth table

A	Out
0	1
1	0

- Multiple libraries

- Layouts

- Number of metal 'tracks'
- More tracks, faster, but larger
- Less tracks – more compact, but slower



- Transistor thresholds (V_{Th}) (for each track height):

- Regular (RVT)
- Low (LVT)
 - Faster, higher power
 - Slower, lower power
- High (HVT)

- Transistor lengths



- Multiple gate sizes within a library

- Symbol

 
 


INVX3,
INVX4,...

- Schematic

  

- Layout

  

Administrivia


- Use this week to finish labs!
- Midterm 2 in 3 weeks
- Bora is away next week



CMOS Logic

Building logic from switches


Series

 

AND

$Y = X$ if A AND B

Parallel

 


OR

$Y = X$ if A OR B

(output undefined if condition not true)

Logic using inverting switches


Series

 

NOR

$$Y = X \text{ if } \overline{A} \text{ AND } \overline{B} \\ = \overline{A + B}$$

Parallel

 


NAND

$$Y = X \text{ if } \overline{A} \text{ OR } \overline{B} \\ = \overline{AB}$$

(output undefined if condition not true)


Static Complementary CMOS

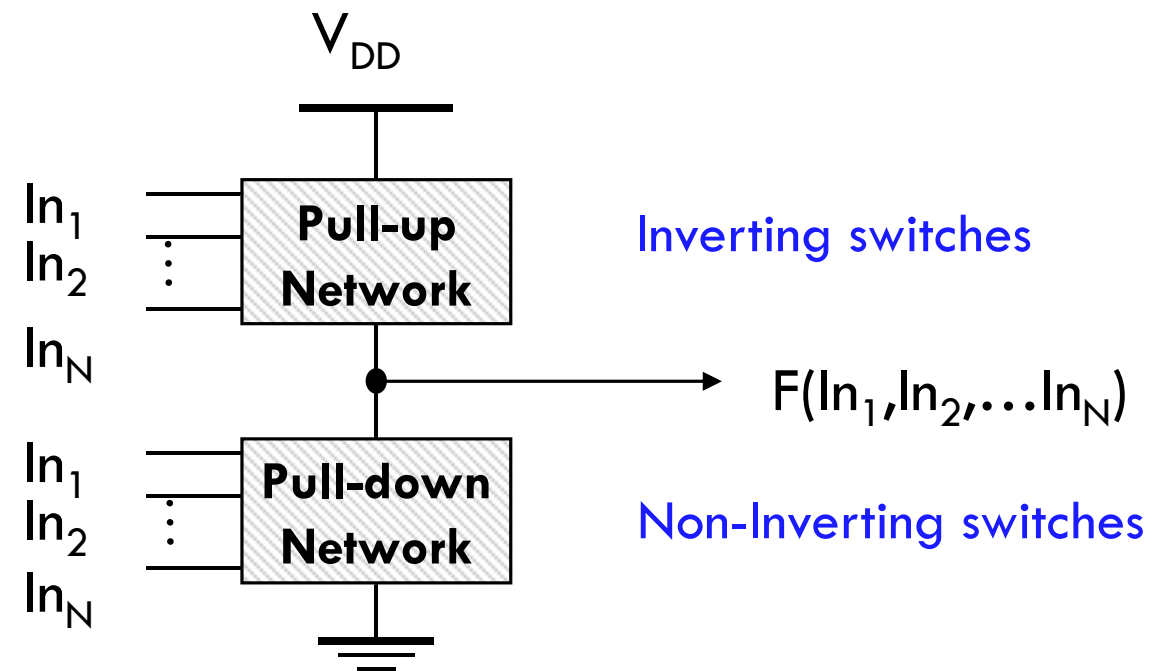

PUN and PDN are **dual** logic networks

PUN and PDN functions are **complementary**

Dual Graphs

 


Complementary CMOS Logic Style

- PUN is the **dual** to PDN
(can be shown using DeMorgan's Theorems)

$$\overline{\overline{A} + \overline{B}} = \overline{\overline{A}} \overline{\overline{B}}$$

$$\overline{\overline{A} \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}}$$

- Static CMOS gates are always inverting

 


AND = NAND + INV

Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

 


- PDN: $G = AB \Rightarrow$ Conduction to GND
- PUN: $F = \overline{A} + \overline{B} = \overline{AB} \Rightarrow$ Conduction to V_{DD}
- $\overline{G(in_1, in_2, in_3, \dots)} \equiv \overline{F(in_1, in_2, in_3, \dots)}$

Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0


Truth Table of a 2 input NOR gate

 

Complex CMOS Gate

$$\text{OUT} = \overline{D + A \cdot (B + C)}$$
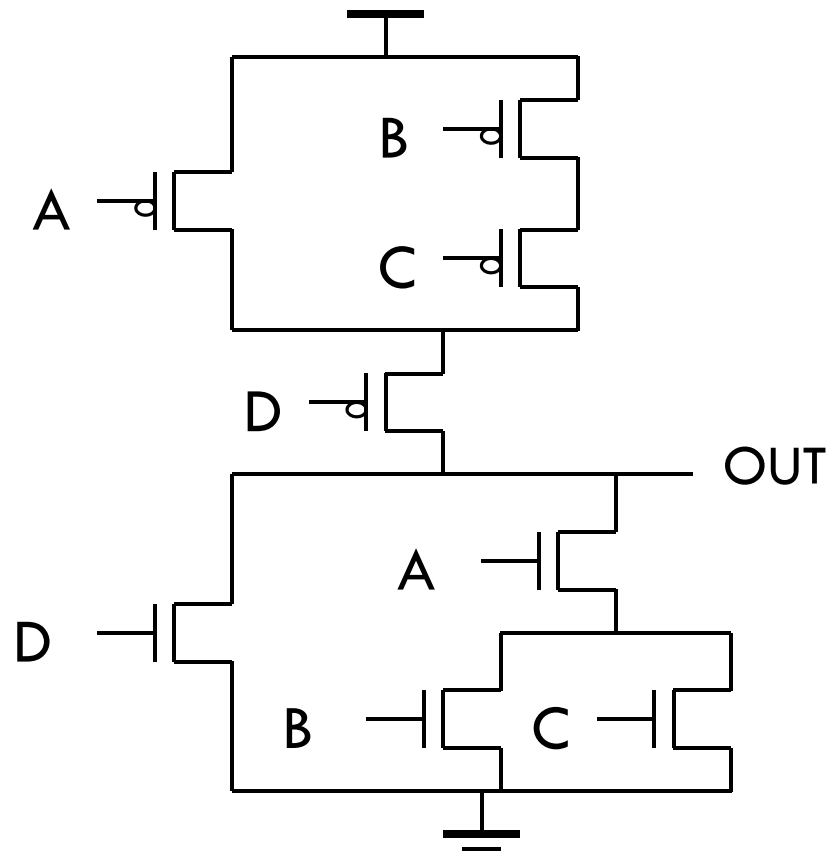
$$\text{OUT} = \overline{D \cdot A + B \cdot C}$$




- Note: In scaled processes max #inputs is 3

Stick Diagrams


Contains no dimensions

Represents relative positions of transistors


Inverter

 


NAND2

 


Stick Diagrams

 



$$X = C \cdot (A + B)$$

 


Logic Graph

 

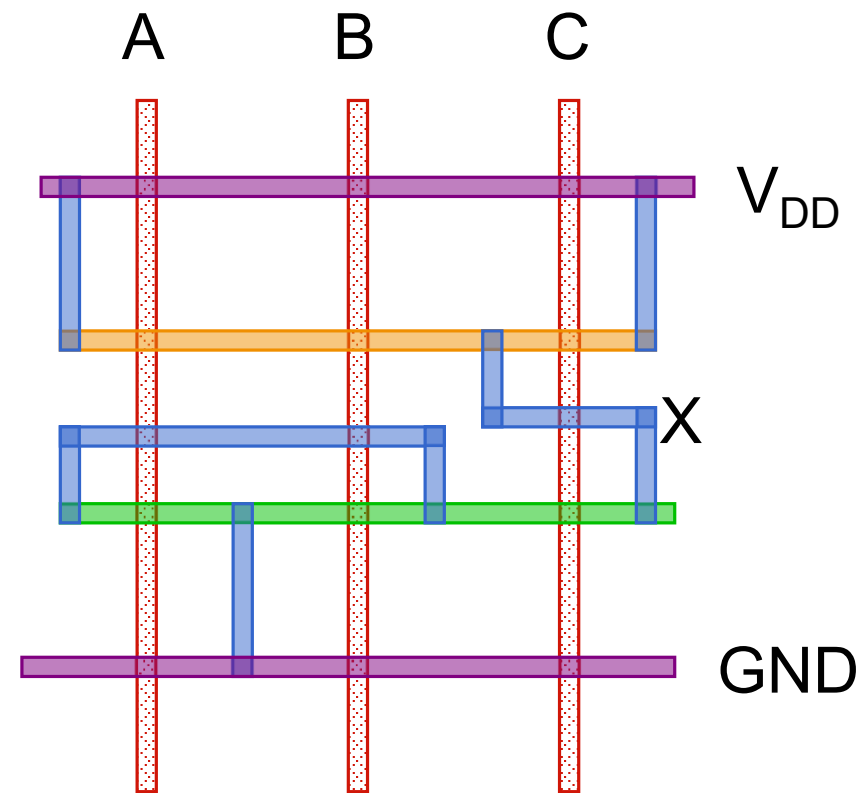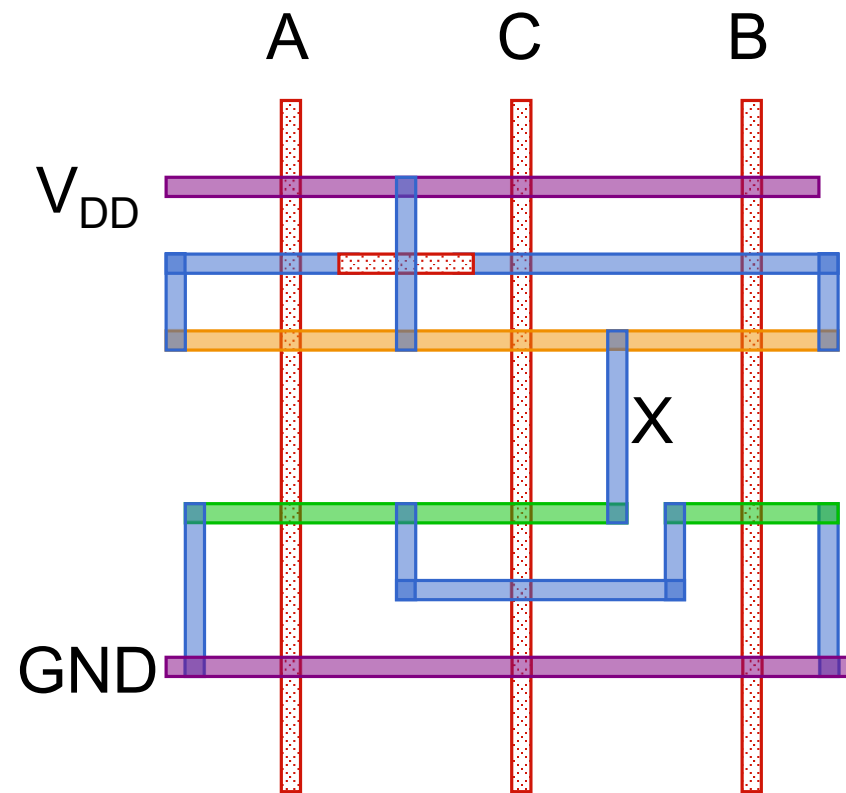Two Versions of $\overline{C \cdot (A + B)}$





Consistent Euler Path

 


A B C


OAI22 Logic Graph

  


Example: $x = \overline{ab+cd}$

 

(a) Logic graphs for $\overline{ab+cd}$


 


(b) Euler Paths $\{a\ b\ c\ d\}$

 


(c) stick diagram for ordering $\{a\ b\ c\ d\}$

Switch Limitations

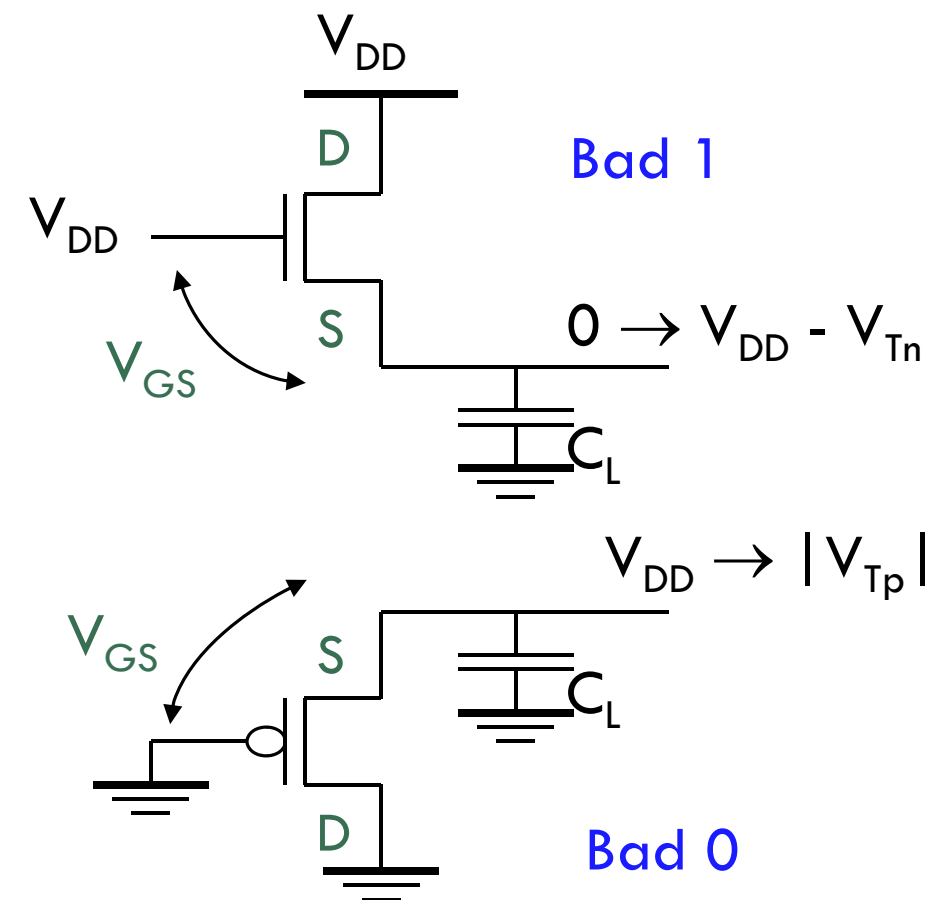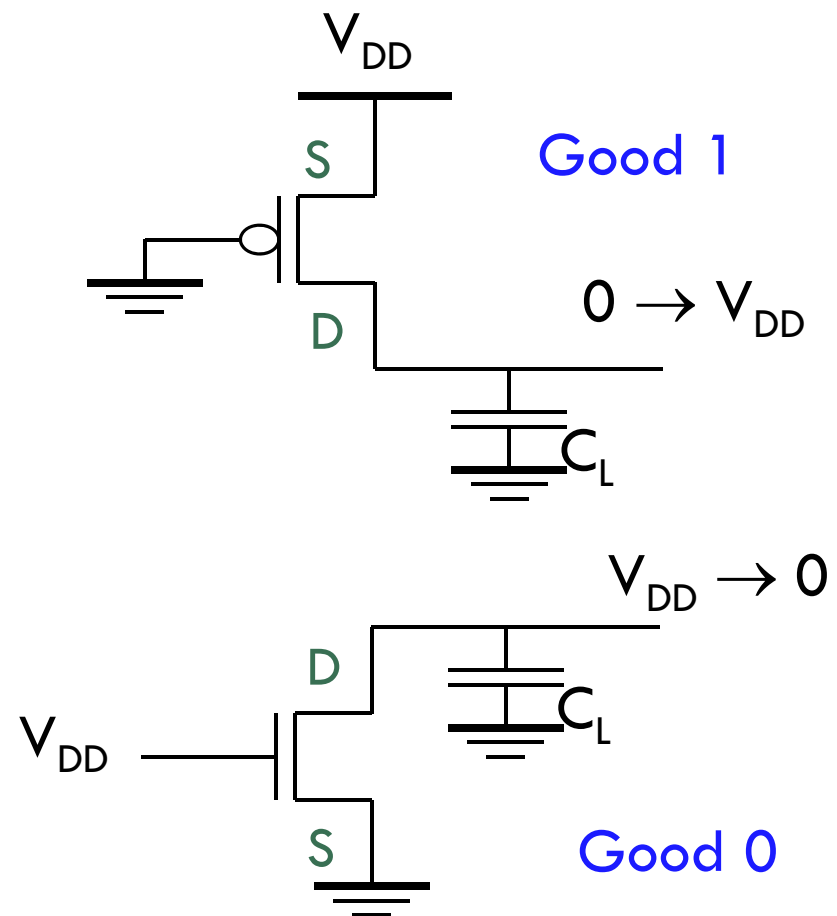


Transmission Gate

 - Transmission gates are the way to build “switches” in CMOS.
- In general, both transistor types are needed:
 - nFET to pass zeros.
 - pFET to pass ones.
- The transmission gate is ‘non-isolating’.




Transmission-Gate Multiplexer

- Implementation

 

Sel	Y
0	A
1	B

 

```
module comb(input a, b, sel,  
            output reg y);  
    always @(*) begin  
        if (sel) y = b;  
        else out = a;  
    end  
endmodule
```


CMOS Multiplexer



Sel	Y
0	A
1	B



CMOS Sizing

Transistor Sizing


- Optimal W_p/W_n

  

- In the past, $W_p > W_n$ (see Rabaey, 2nd ed)
- In modern processes (finFET), $W_p = W_n$

Gate Sizing

 - Doubling the gate size (by doubling W_s):




- Doubles C_{in}
- Halves equivalent gate resistance
- Doubles C_p





CMOS Delay

Inverter Delay

- How to time this?



 


  - Each gate has an R_{eq} and drives C_{in} of the next gate




Inverter Delay




- High-to-low

   
 
$$t_{p,HL} = (\ln 2)\tau = 0.7 R_{eq,n}(C_p + C_L)$$



Inverter Delay

   

$$t_{p,LH} = (\ln 2)\tau = 0.7 R_{eq,p}(C_p + C_L)$$

Summary

- CMOS allows for convenient switch level abstraction
- CMOS pull-up and pull-down networks are complementary
- Transistor sizing affects gate performance
- Delay is a linear function of R and C