


# EECS 151/251A: Discussion 2

Noise Margins, RTL Design, Simulation

---


9/5/2019

# The CMOS Inverter

 


- NMOS turns 'on' when  $V_{in} > V_{th,n}$
- PMOS turns 'on' when  $V_{DD} - V_{in} > V_{th,p}$
- We assume each device has an on ( $R_{on}$ ) and off ( $R_{off}$ ) resistance

# Voltage Transfer Characteristic

 


- $V_{OL} = 0$  and  $V_{OH} = V_{DD}$  are the nominal low and high voltage levels
- $V_M$  - the switching threshold is a function of the relative 'strength' of the NMOS and PMOS
- Draw a VTC for  
 $V_{DD} = 1, V_{th,n} = 0.2, V_{th,p} = 0.3, R_{on,n} = 10k\Omega, R_{on,p} = 20k\Omega$

# Noise Margins

 


- $V_{IL}$  and  $V_{IH}$  - bound the high-gain region of the VTC (unstable, high noise influence)
- In the undefined region the inverter acts like an amplifier and amplifies noise on the input and supply

# Regeneration

 


- Regenerative inverter has a VTC with low-gain regions around supplies and a high-gain region in between

# Inverter Chain

 

A chain of inverters

 

- A chain of CMOS inverters is regenerative, due to their VTCs
- As long as the input to the chain is not in the undefined region, the output will swing from rail to rail

- We're going over the Verilog Primer Slides and some slides from last semester's Verilog discussion.

# Simulation

We can test RTL via simulation before putting it on the FPGA or fabricating an ASIC.

Let's test a simple adder circuit (demo time), then a freerunning counter, and some other stuff.