

Discussion 8

Pipeline Hazards, MOS Switch, CMOS Logic

Pipeline hazards

- Structural Hazard

- An instruction in the pipeline may need a resource being used by another instruction in the pipeline
- Solution: Stalling newer instruction, or adding more hardware

- Data Hazard:

- An instruction may depend on a data value produced by an earlier instruction

- Control Hazard (branches, exceptions)

- An instruction may depend on the next instruction's address

Structural hazard


- Memory access
 - Register files have multiple ports (2 read, 1 write)
 - Separate instruction memory and data memory

Data Hazard


$x1 \leftarrow x0 + 10$

$x4 \leftarrow x1 + 3$

$x5 \leftarrow x1 + 5$

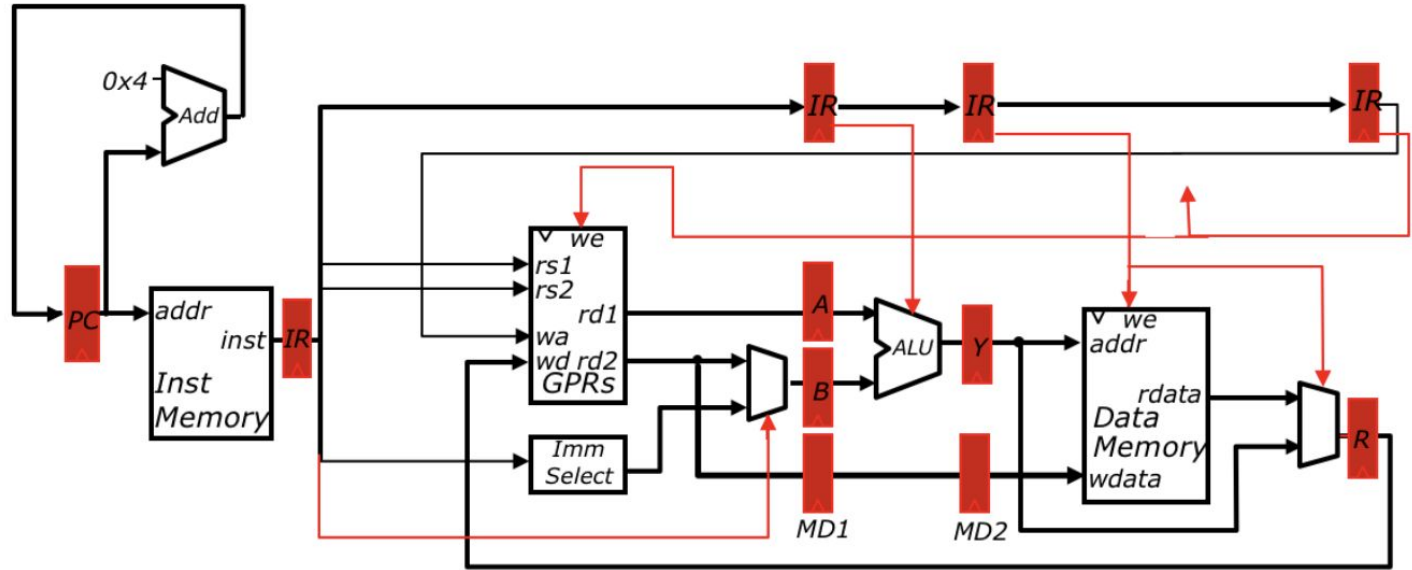


Data Hazard

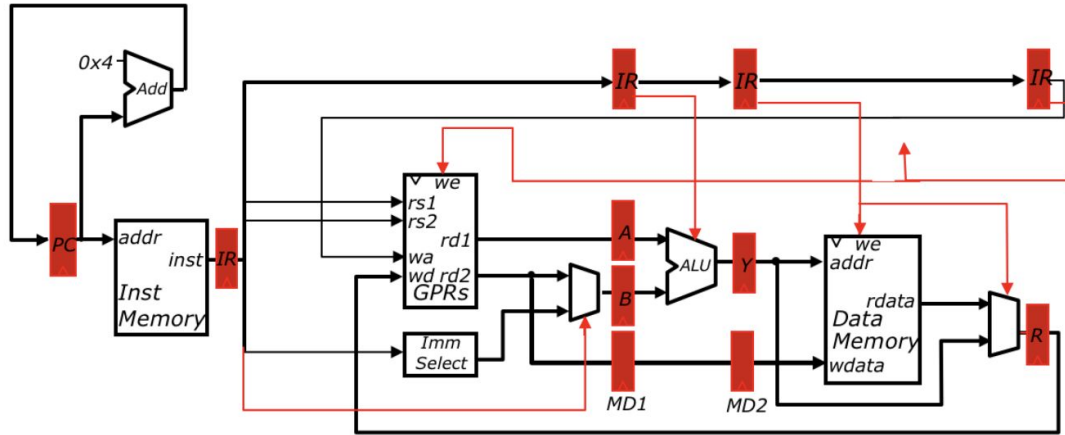


Time	$x1 \leftarrow x0 + 10$	$x4 \leftarrow x1 + 3$	$x5 \leftarrow x1 + 5$
t0	IF		
t1	ID	IF	
t2	EX	ID	IF
t3	MA	?	ID
t4	WB		?
t5			
t6			
t7			

Data Hazard: Stalling

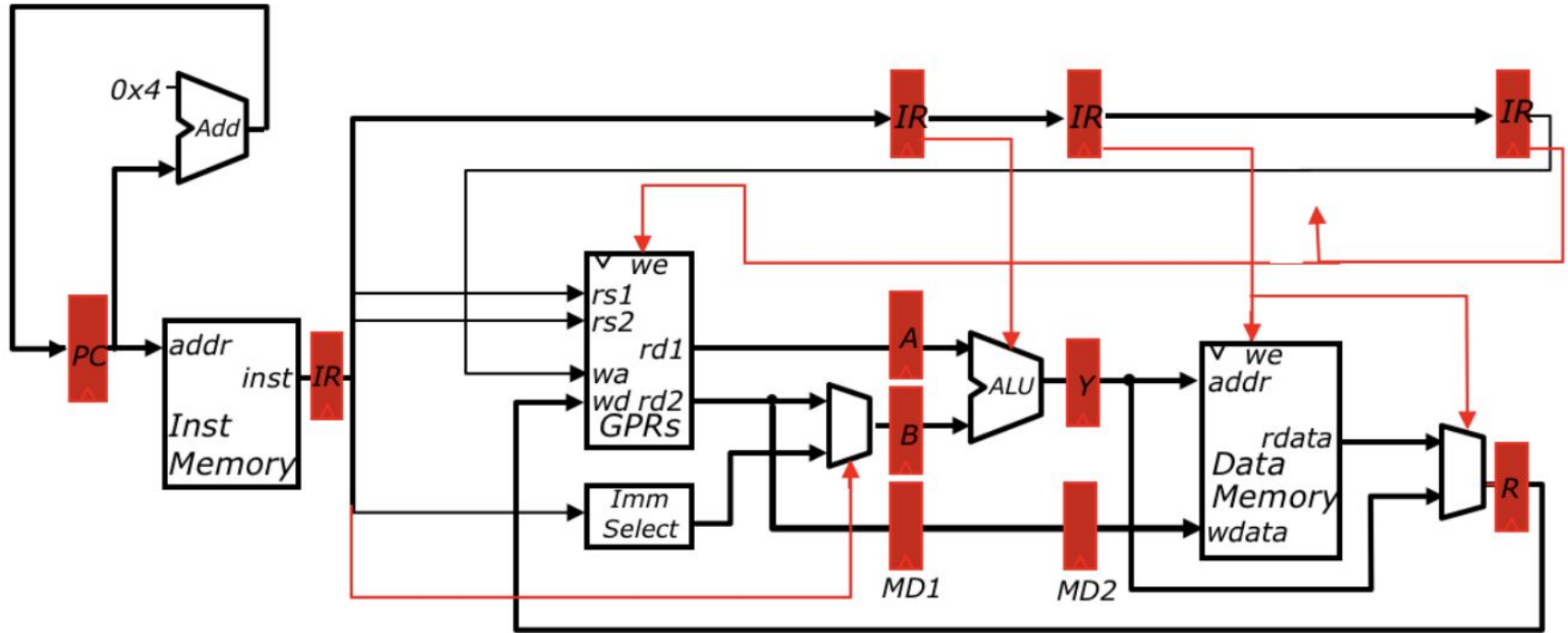


Data hazard: stalling

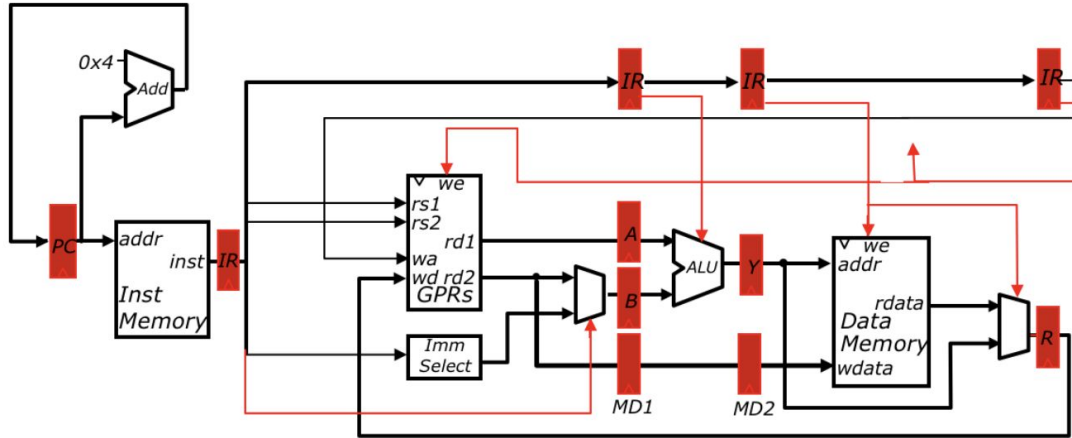


Assume register file can be written and read at the same time

Time	$x1 \leftarrow x0 + 10$	$x4 \leftarrow x1 + 3$	$x5 \leftarrow x1 + 5$
t0	IF		
t1	ID	IF	
t2	EX	ID	IF
t3	MA	ID	IF
t4	WB	ID	IF
t5		ID	IF
t6		EX	ID
t7		MA	EX

Data Hazard: forwarding

 

Control Hazard: jump

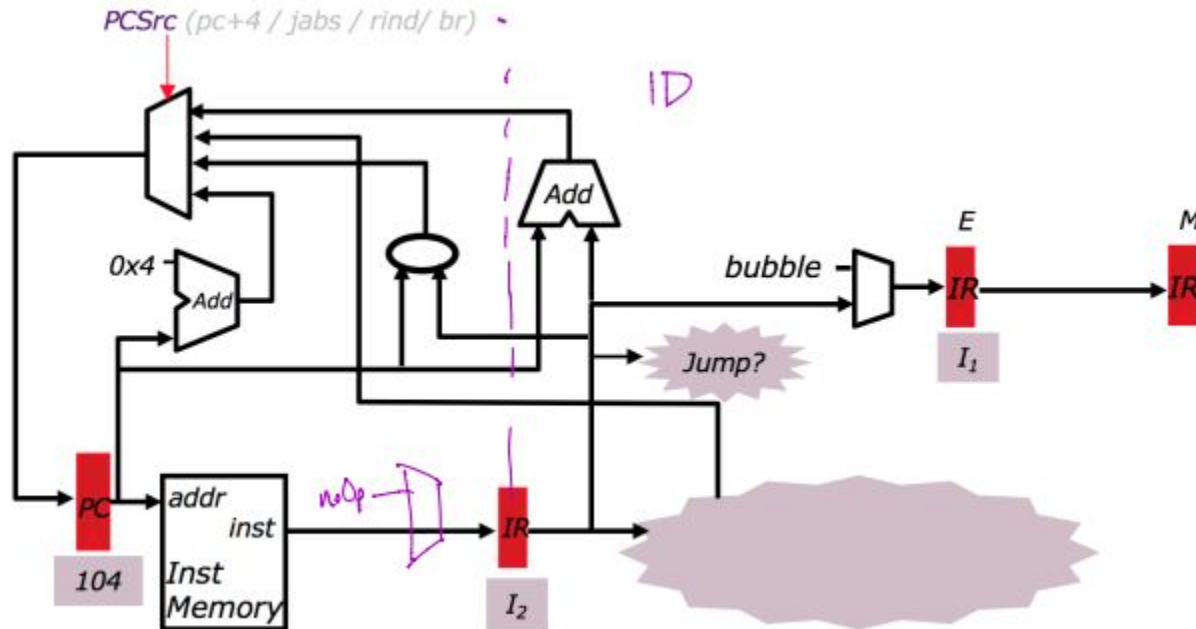

Example


096	ADD
100	J 304
104	ADD
.....	
304	ADD

Automatically fetched into pipeline, need to kill it

Control Hazard: conditional branch

 Example


```
096    ADD
100    BEQ x1, x2, 200
104    ADD
108    ADD
112    ADD
```



Forwarding vs. Stalling


- There are many ways to implement a combination of forwarding or stalling in a pipelined datapath
- You have to find the right tradeoff between a longer critical path, balancing pipeline stage delays, and pipeline stalled cycles
- Consider an Load -> ALU dependency
 - Could forward the load result the same cycle and incur a long critical path but have no stall cycles
 - Could stall the ALU instruction 1 cycle until the load result is in a pipeline register but get a shorter critical path
 - What is better? Try both and see!
 - Intuitively the longer critical path would make the pipeline stages very unbalanced and would hurt max frequency (f_{max}) more than it would help latency (CPI)
- Iron Law: Execution time = $\# \text{ Insns} * \text{CPI} * T_{clk}$

HW5 #3 Branch Clarification

 

- What's the resolution latency of a branch instruction for the 5-stage pipeline from lecture? How many instructions need to be killed?


HW5 #3 Branch Clarification

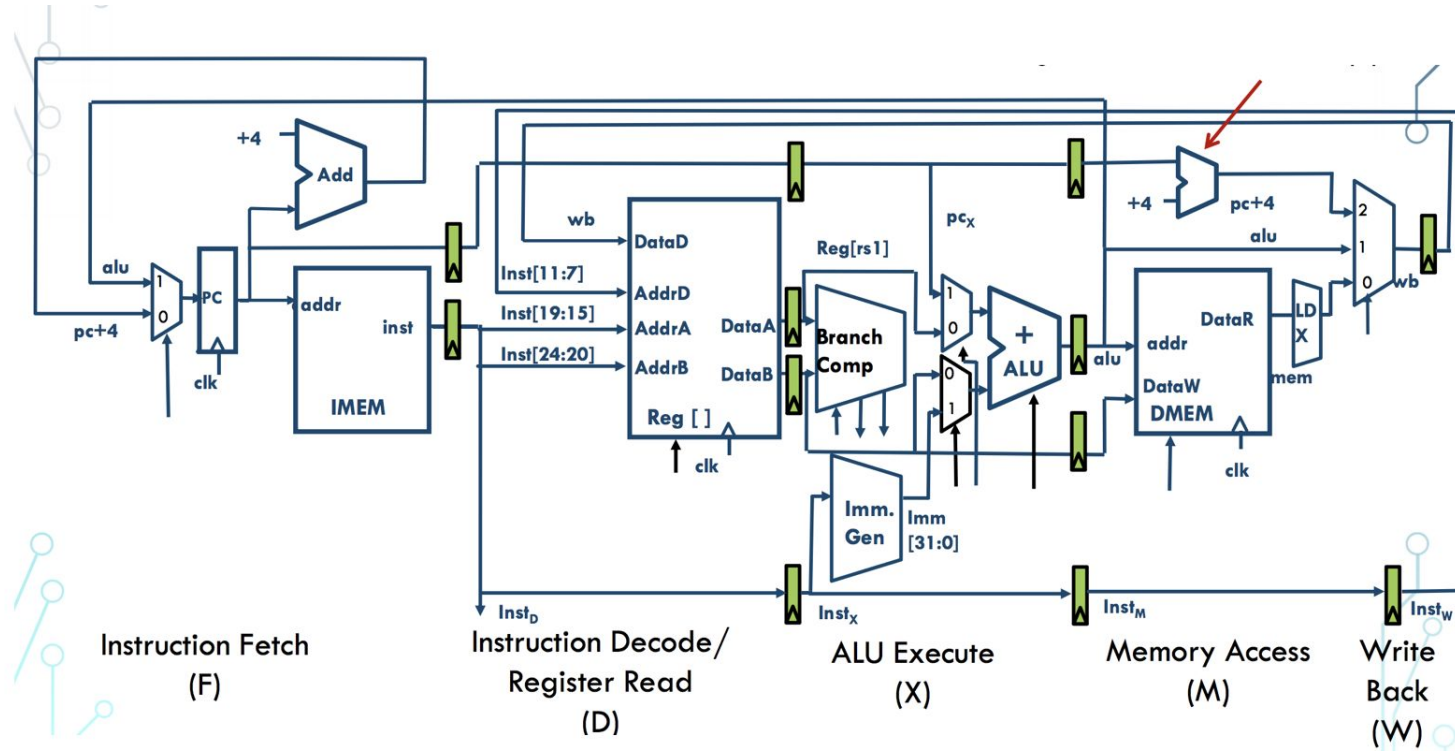


- How should we implement a branch always taken naive predictor? Waiting until the ALU for the branch target address doesn't make sense.

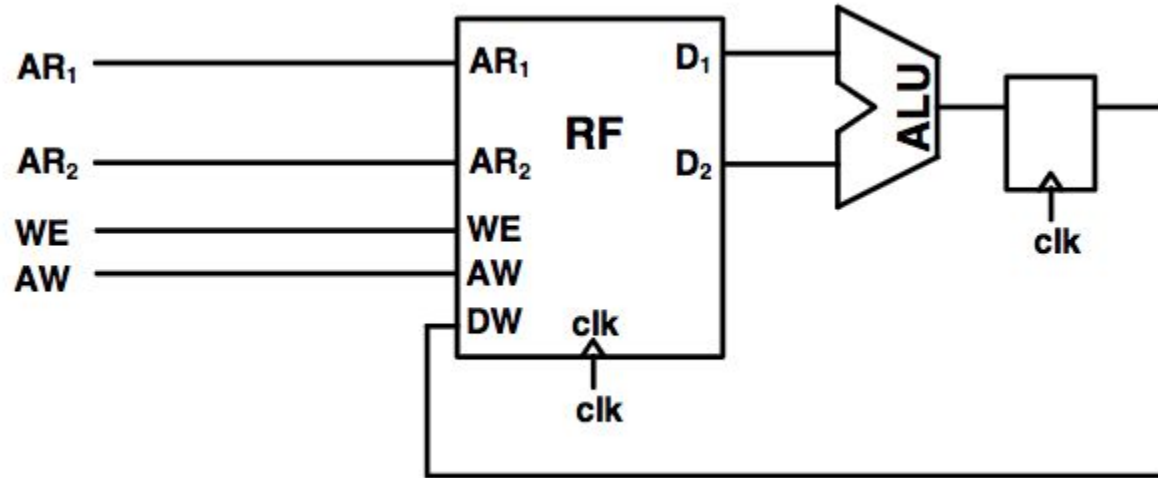Example

Shown below is a portion of a prototype design for a pipelined CPU's datapath that uses a register file with **synchronous reads and writes**. However, even ignoring any potential data hazards, this design does not function correctly - in particular, register type instructions. Explain what the error is caused by and add any extra components necessary to correct the design.




Example

 


Example

Now this register file has synchronous writes with asynchronous reads. Add appropriate forwarding to eliminate all data hazards.

 


Example 2

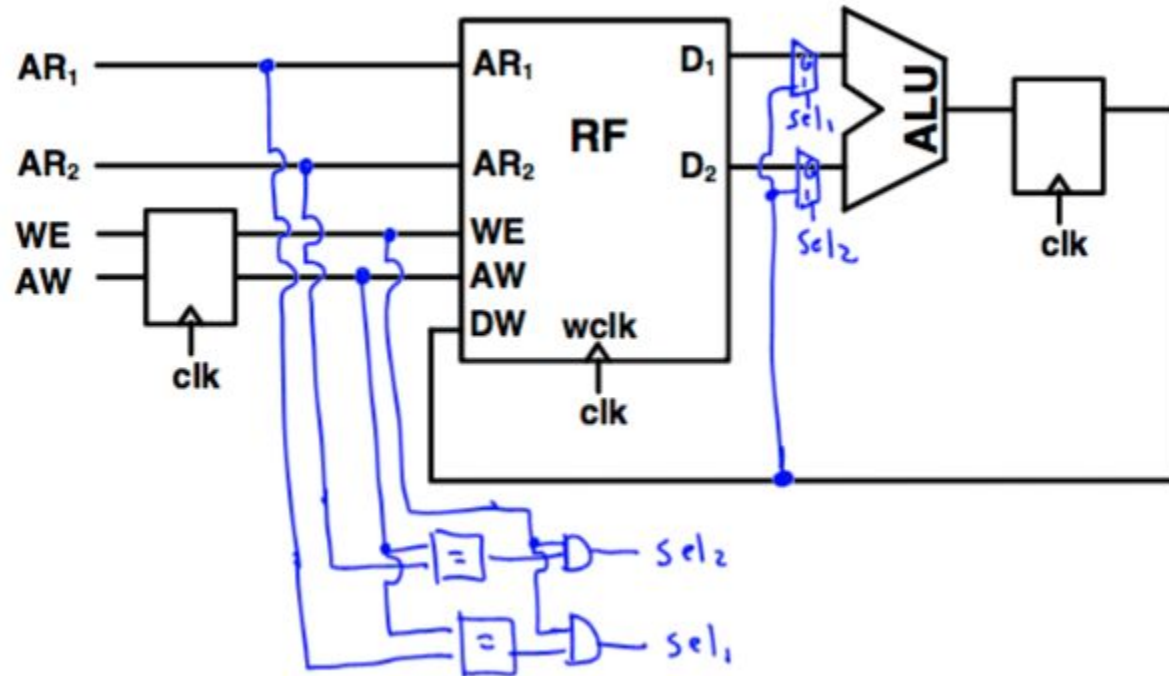


MOS Switch

MOS Transistor

 


A Switch!

 


- V_{GS} controls the switch
 - (it also charges the channel capacitor)

MOS Switch



ON/OFF Model

 

“More Realistic” Model

 


MOS Switch

  




- Source of NMOS always at lower voltage
- Source of PMOS always at higher voltage
- The 'effective' source node can change depending on the voltage at the MOS' terminals

Switch Logic

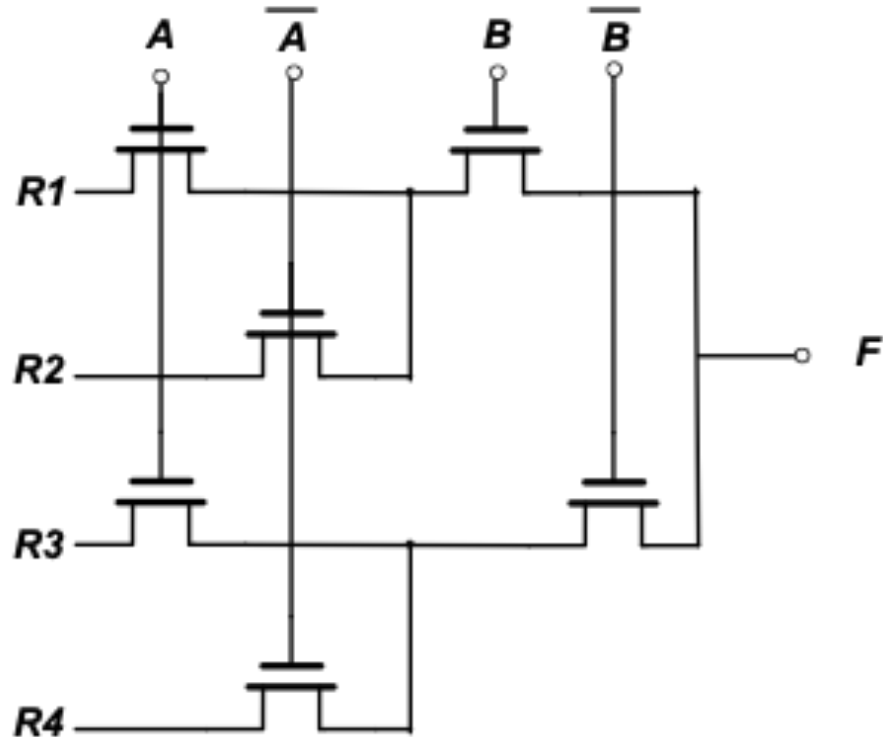


CMOS Inverter

- Schematic

   
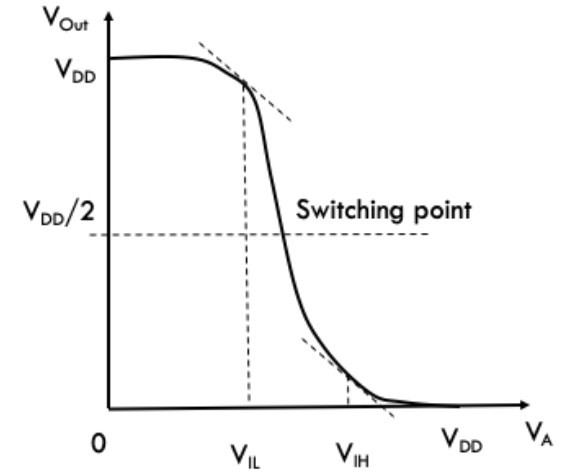
$$\begin{aligned} V_{OL} &= 0 \\ V_{OH} &= V_{DD} \end{aligned}$$




Inverter VTC

[7pts/11pts] Voltage Transfer Characteristics (VTCs).

The technology has the following parameters: $V_{th,N} = 0.2V$ and $|V_{th,P}| = 0.3V$, $R_n = 2k\Omega * \mu m$, $R_p = 3k\Omega * \mu m$ at $V_{dd} = 1V$. Draw the voltage transfer characteristic (V_{out} vs V_A) of the gates below with $W_p = W_n = 1\mu m$.

 - (a) [4pts] Draw the VTC and determine V_{OL} , V_{IL} , V_{OH} , V_{IH} and noise margins NM_H and NM_L .



Remember: Noise margin high:

$$NM_H = V_{OH} - V_{IH}$$

Noise margin low:



$$NM_L = V_{IL} - V_{OL}$$

Inverter VTC


[7pts/11pts] Voltage Transfer Characteristics (VTCs).

The technology has the following parameters: $V_{th,N} = 0.2V$ and $|V_{th,P}| = 0.3V$, $R_n = 2k\Omega * \mu m$, $R_p = 3k\Omega * \mu m$ at $V_{dd} = 1V$. Draw the voltage transfer characteristic (V_{out} vs V_A) of the gates below with $W_p = W_n = 1\mu m$.

 
 
- (a) [4pts] Draw the VTC and determine V_{OL} , V_{IL} , V_{OH} , V_{IH} and noise margins NM_H and NM_L .




Inverter VTC

 

Inverter VTC

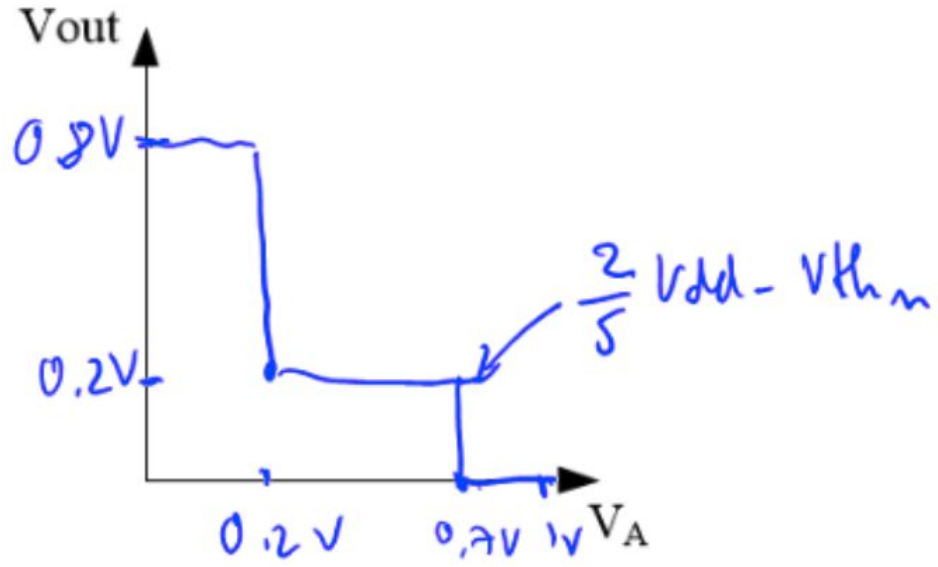
 


CMOS Logic

 

PUN and PDN are **dual** logic networks

  PUN and PDN functions are **complementary**



CMOS Logic

XNOR:

CMOS Logic

AND2: