

# Discussion

Karnaugh Maps, Minimization, & FSMs

# Karnaugh Maps

- Visual method for boolean simplification
- Makes use of 2 important boolean identities:


$$(1 + A) = 1$$

$$(A + \bar{A}) = 1$$

- Leverages gray coding to organize neighboring minterms
  - Adjacent minterms only differ by a single bit!


2 variable Karnaugh map
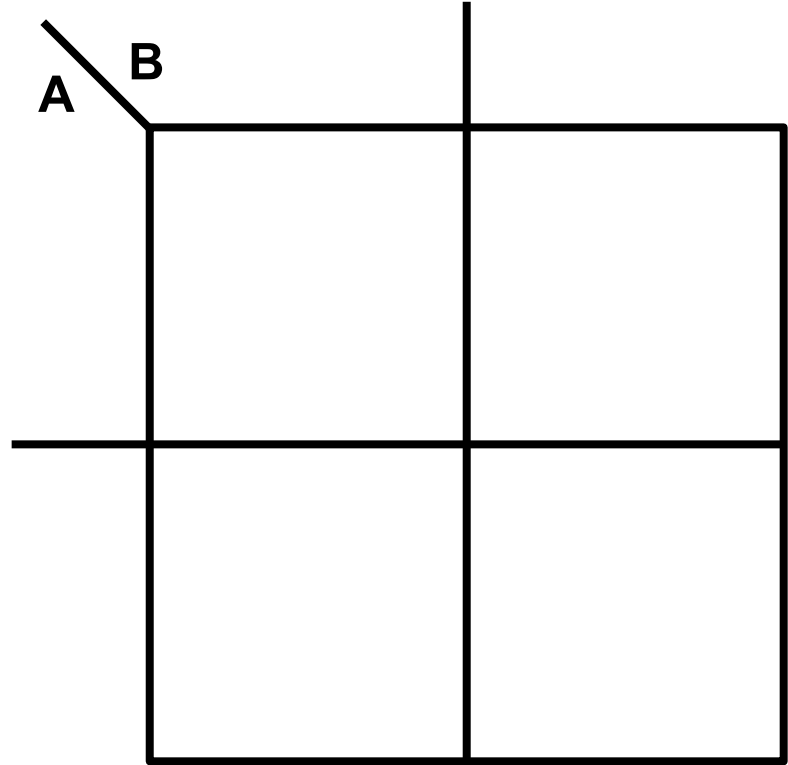
$$F(A,B) = \overline{A}B + \overline{A}$$




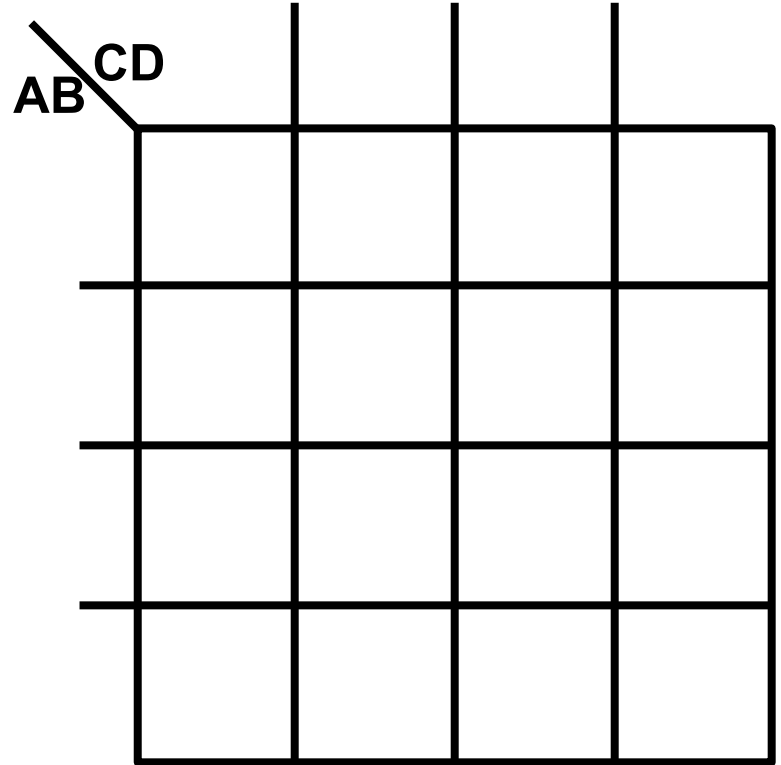
## 4 variable Karnaugh map


$$\begin{aligned} F(A,B,C,D) = & \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}C\bar{D} + \\ & \bar{A}B\bar{C}\bar{D} + \bar{A}B C\bar{D} + \\ & A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} + \\ & A\bar{B}C D + A\bar{B}\bar{C}D + \\ & ABCD \end{aligned}$$


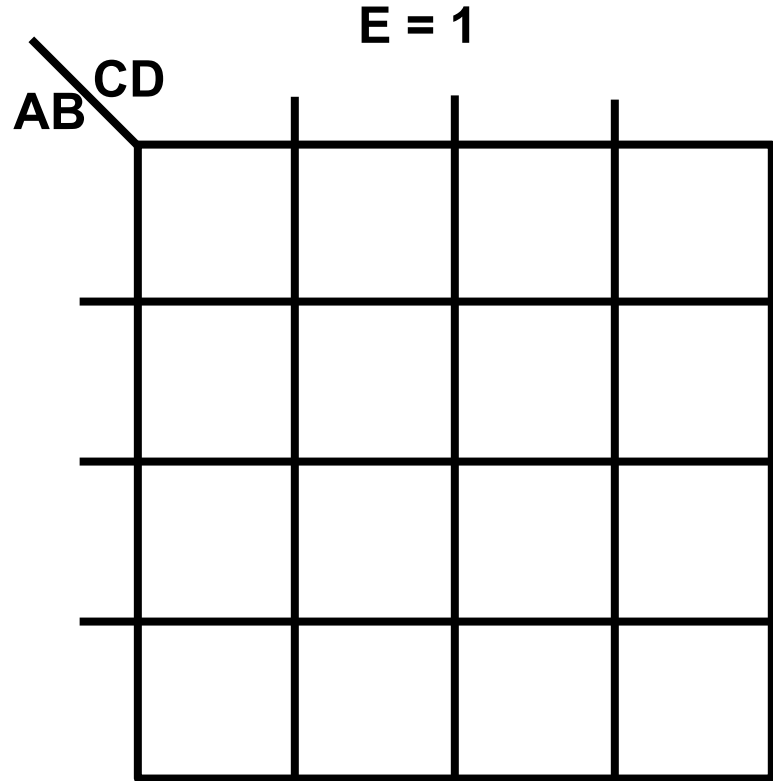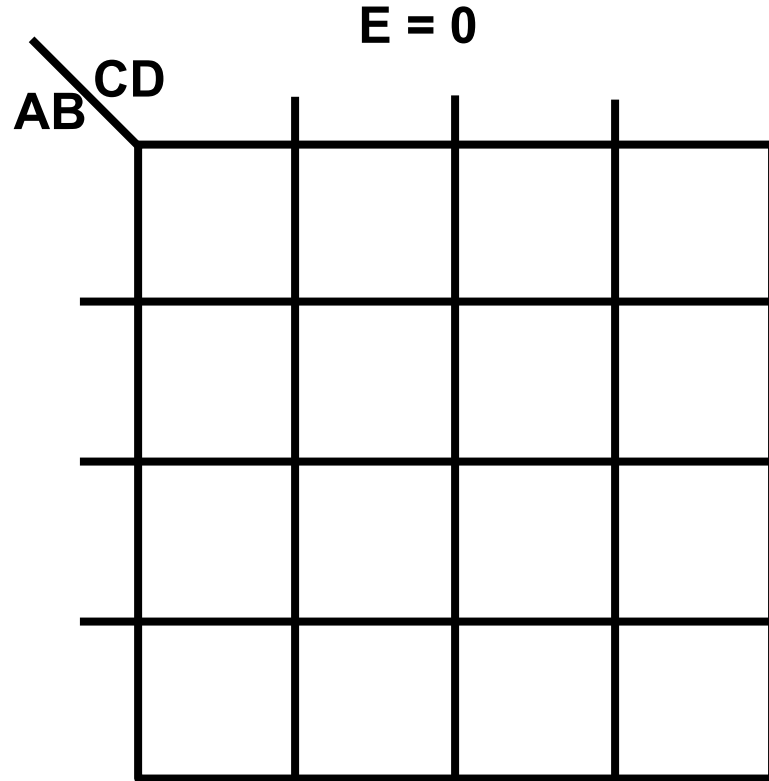
# 5 Variable Karnaugh Map!! (The Bad Way)



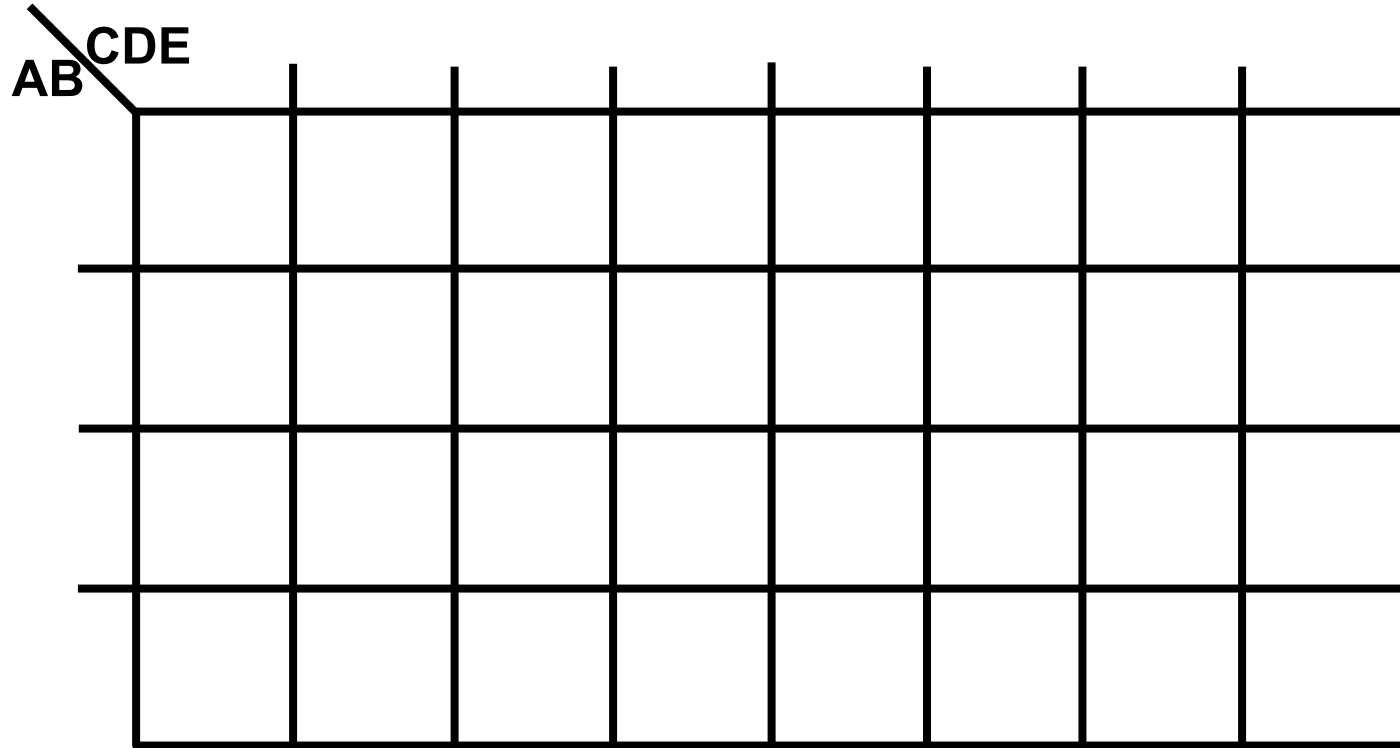
# 5 Variable Karnaugh Map!! (The Good Way)



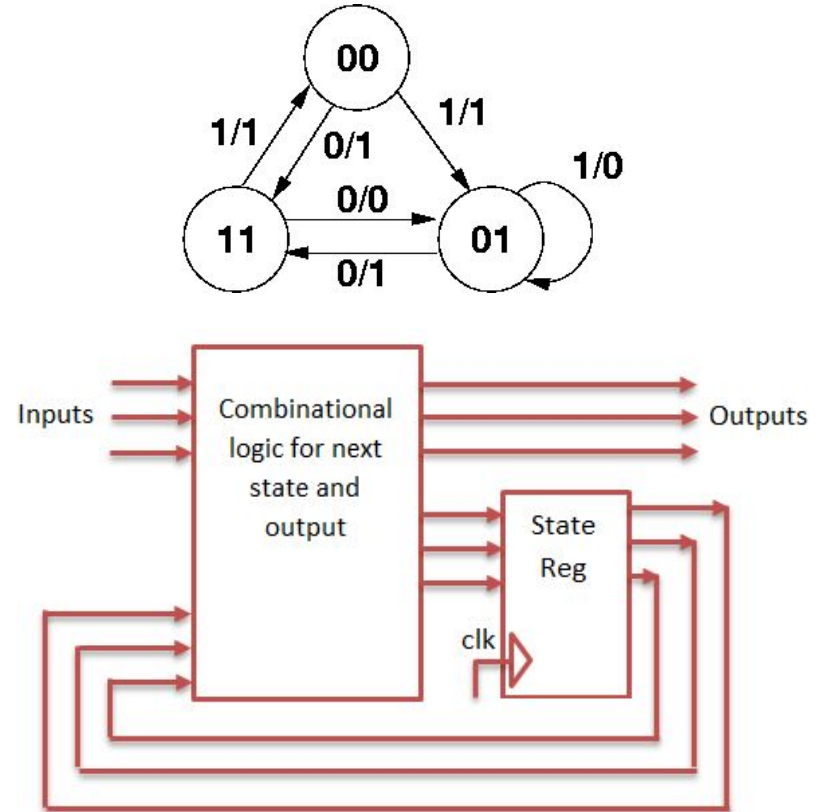
# Finite State Machines

- What are they used for?
- Mealy vs. Moore?
- States are the memory!
- Can be represented in many ways
  - Bubble diagrams
  - Tables
  - Case statements in verilog



# Building transition table

Input	State	Next State	Output

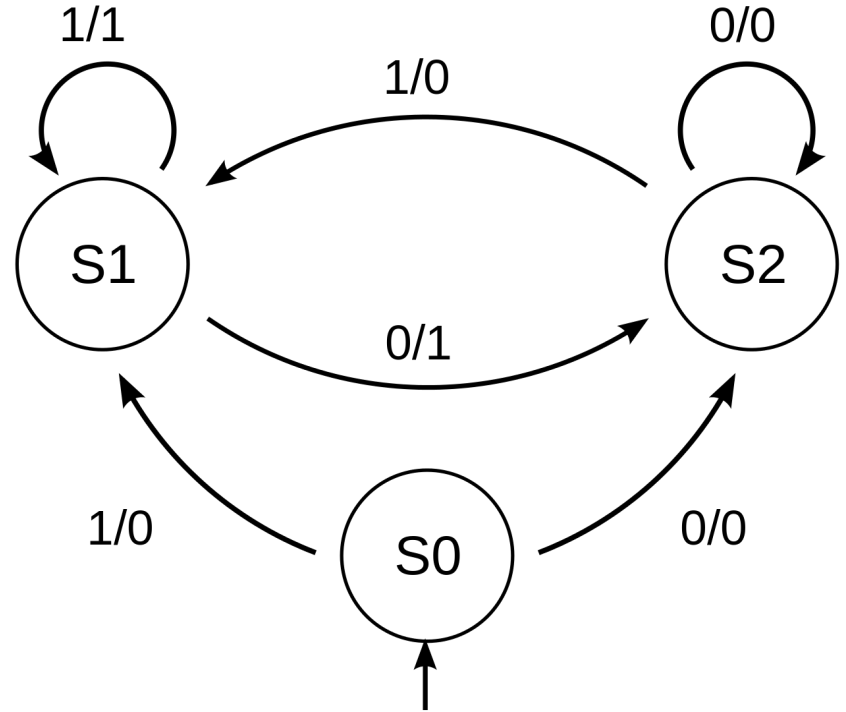



# Building the circuit

Input	State	Next State	Output
0	S0	S2	0
1	S0	S1	0
0	S1	S2	1
1	S1	S1	1
0	S2	S2	0
1	S2	S1	0

Equations:

S1 =

S2 =

Output =

# Building a Bubble Diagram

Input	State	Next State	Output
Timer	Green	Green	N/A
Button	Green	Yellow	N/A
Timer	Yellow	Red	N/A
Timer	Red	Green	N/A