

EECS151 : Introduction to Digital Design and ICs

Lecture 18 – SRAM

Bora Nikolić and Sophia Shao



Nvidia Shrinks AI ‘Supercomputer’ to Credit Card Size

Nov. 6, 2019. Nvidia’s Jetson Xavier NX board is smaller than a credit card and provides 1.4 TOPS/W (Image: Nvidia)




Review

- Flip-flops are edge-triggered
- Long timing paths need to meet the setup time of receiving flip-flop
- Short timing paths have to be longer than hold time + $t_{\text{clk-Q}}$
- Flip-flops are often designed as latch pairs




Setup and Hold Times

Setup and Hold Times

 


(a)

 

(b)

Setup-Hold Time Illustrations

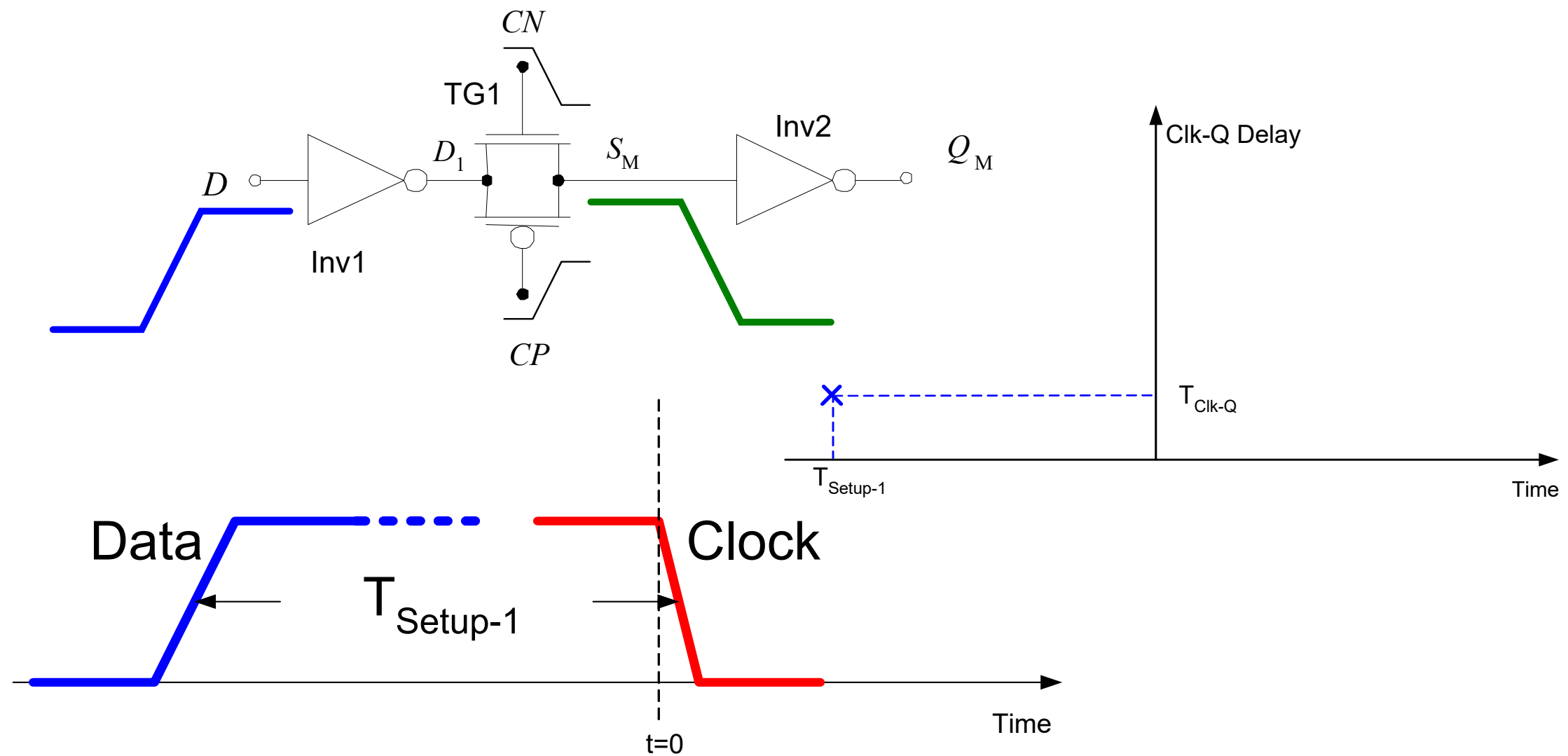Circuit before clock arrival (Setup-1 case)







Flip-Flops

Types of Flip-Flops

Latch Pair
(Master-Slave)

 



Pulse-Triggered Latch

 

Transmission Gate Flip-Flop


- Two back-to-back latches

- In ASAP7

  


Aside: Inverter Fork

 - Often found in flip-flops: equalize C_k , C_{kb} delays





Clk-Q, Setup and Hold Times

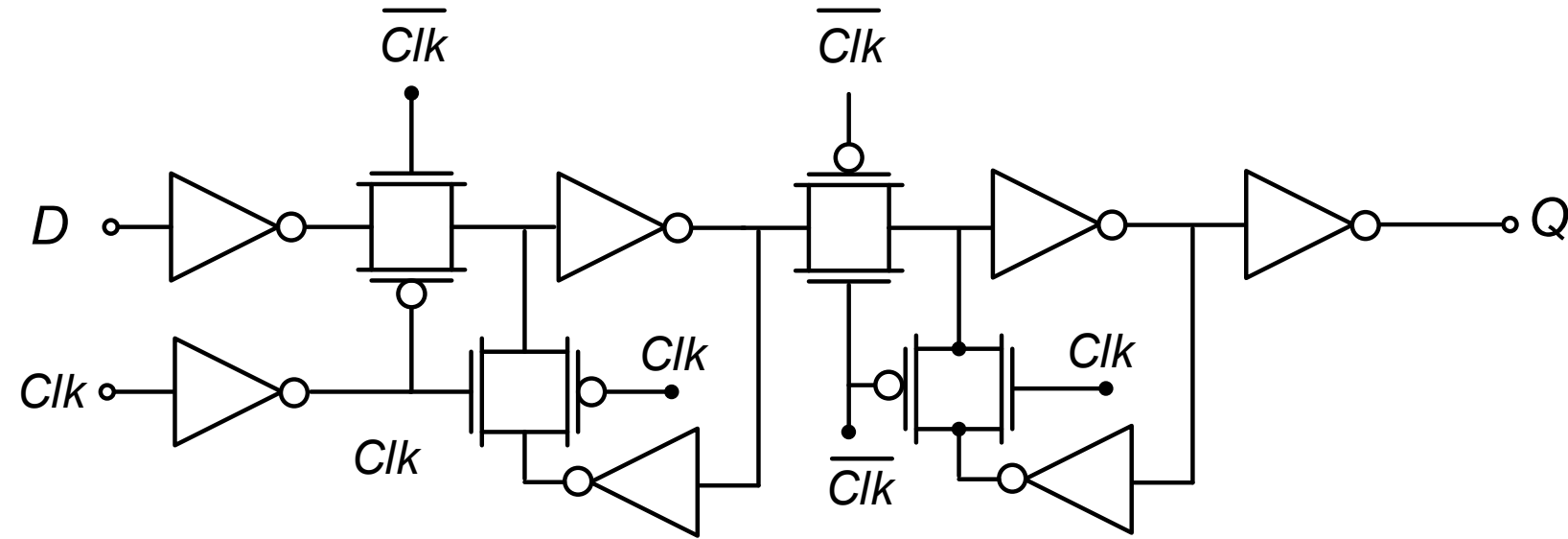


Scan

  - Scan input is used for functional test of the chip




 - During test, a desired pattern is 'scanned' into the chain of flip-flops



Set, Reset

 - Set and reset can be synchronous or asynchronous
 - Always watch for additional timing paths!



D-flip-flop with **synchronous** reset

```
module dff_sync_clear(  
  input d, r, clk,  
  output reg q);  
  
  always @(posedge clk)  
  begin  
    if (!r) q <= 1'b0;  
    else q <= d;  
  end  
endmodule
```

always block entered only at each positive clock edge



D-flip-flop with **asynchronous** reset

```
module dff_async_clear(  
  input d, r, clk,  
  output reg q);  
  
  always @(negedge r or posedge clk)  
  begin  
    if (!r) q <= 1'b0;  
    else q <= d;  
  end  
endmodule
```


always block entered immediately when (active-low) r is asserted

Flip-Flop Timing Characterization

- Combinational logic delay is a function of output load and input slope
- Sequential timing (flip-flop):
 - $t_{\text{clk-q}}$ is function of output load and clock rise time
 - t_{su} , t_{H} are functions of D and Clk rise/fall times

Registers, Register files

 - Register is often built out of flip-flops





- Register file can be built out of registers
 - Ok for small register files
 - Large register files are generally built with latches and custom designed (like memory arrays)



SRAM


Random Access Memory Architecture

  - **Conceptual: Linear array of addresses**
 - Each box holds some data
 - Not practical to physically realize
 - millions of 32b/64b words
- **Create a 2-D array**
 - Decode Row and Column address to get data




Basic Memory Array

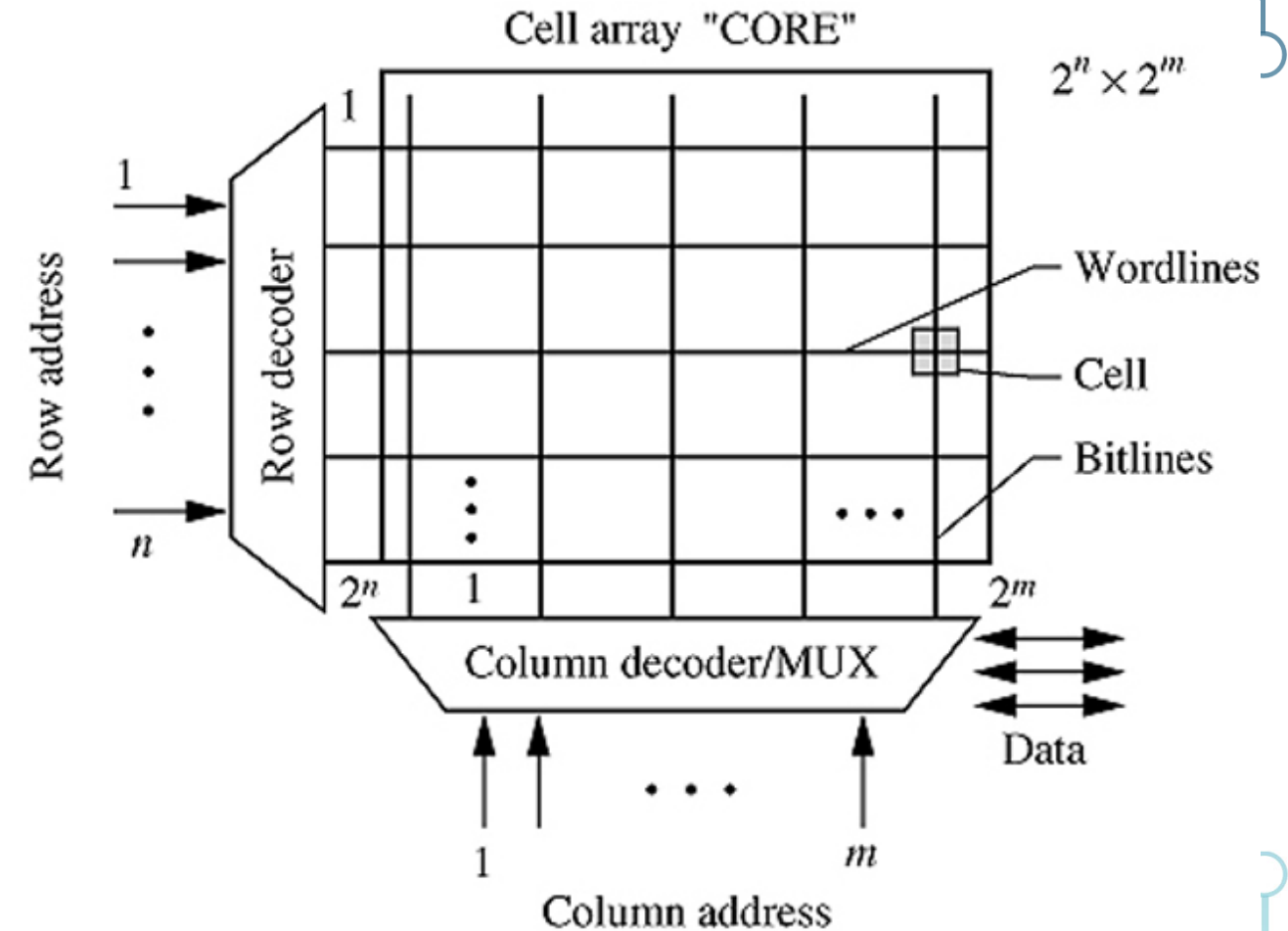- CORE
 - Wordlines to access rows
 - Bitlines to access columns
 - Data multiplexed onto columns
- Decoders
 - Addresses are binary
 - Row/column MUXes are 'one-hot' - only one is active at a time




Basic Static Memory Element

 


- If D is high, \overline{D} will be driven low
 - Which makes D stay high
- Positive feedback
- Same principle as in latches

Positive Feedback: Bi-Stability

- As in latches

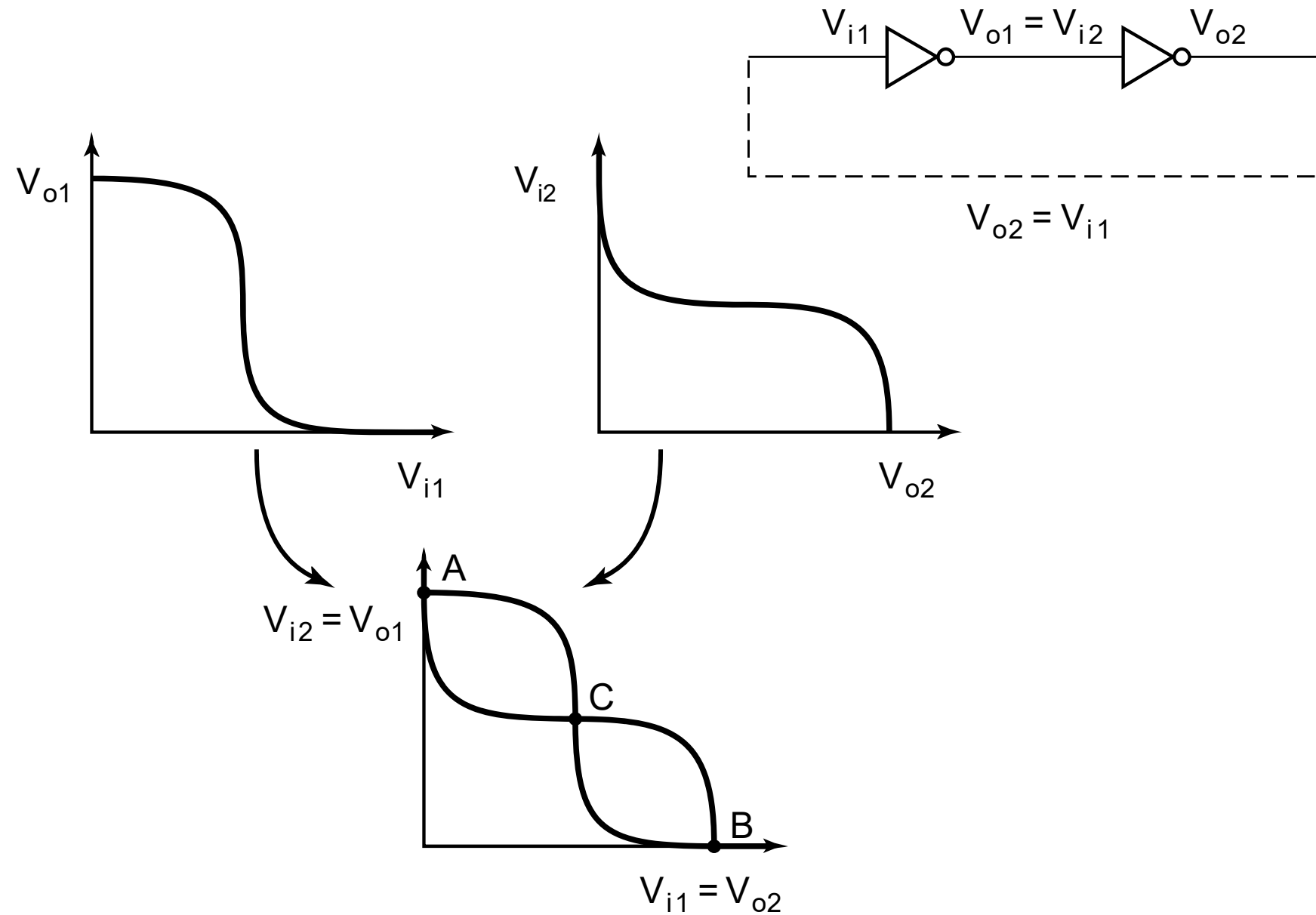


Writing into a Cross-Coupled Pair

 


- This is a 5T SRAM cell
 - Access transistor must be able to overpower the feedback; therefore must be large
 - Easier to write a 0, harder to write 1
- Can implement as a transmission gate as well; single-ended 6T cell
- There is a better solution...

SRAM Cell

 

Since it is easier to write a 0 through NMOS, write only 0s, but on opposite sides!
When reading, measure the difference


6-transistor CMOS SRAM Cell

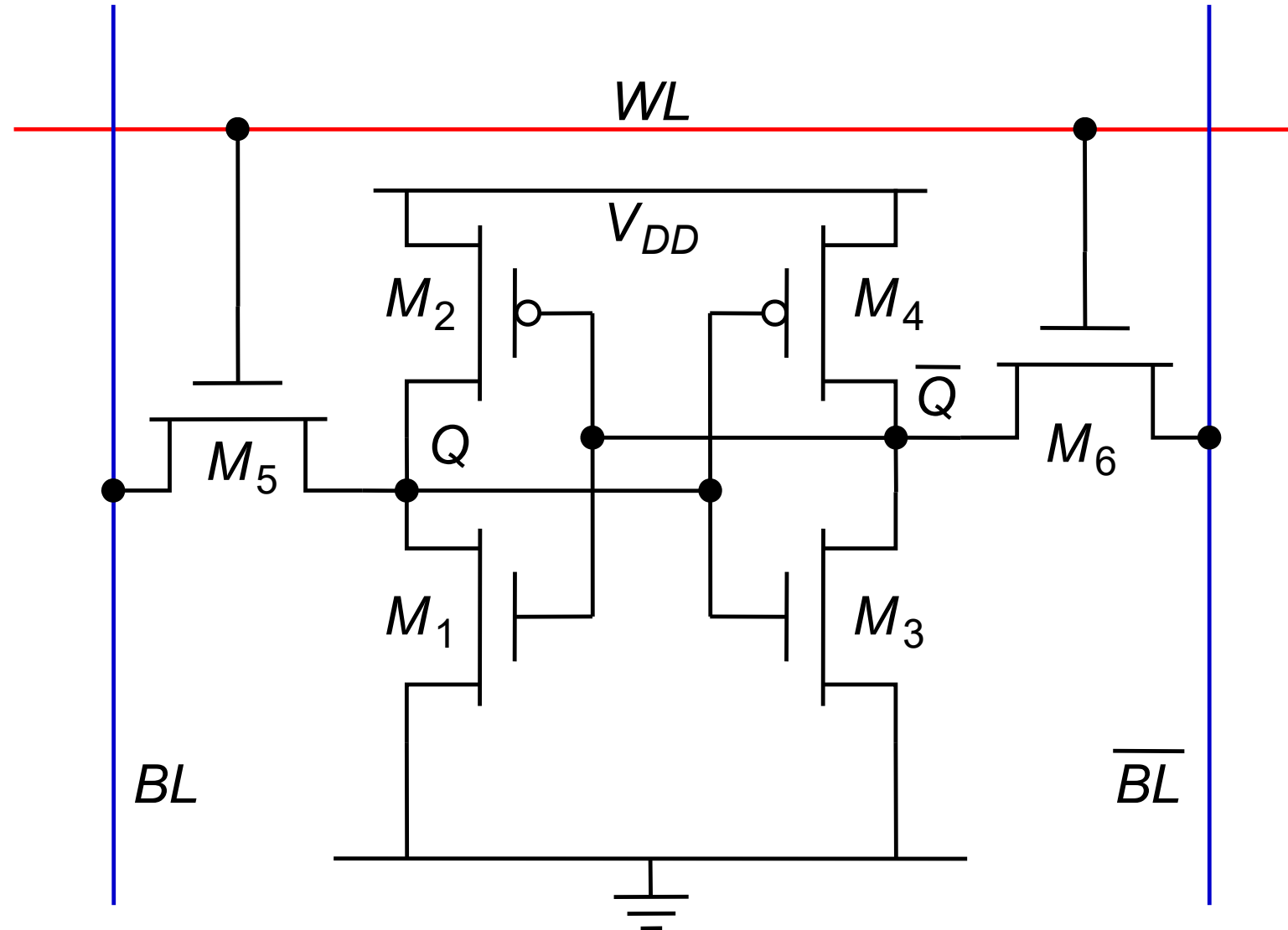


- Wordline (WL) enables read/write access for a row
- Data is written/read differentially through shared BL , \bar{BL}

SRAM Operation

Write

 


Hold

 

SRAM Operation

Read

 


SRAM read is non-destructive

- Reading the cell should not destroy the stored value


Sizing SRAM Cell

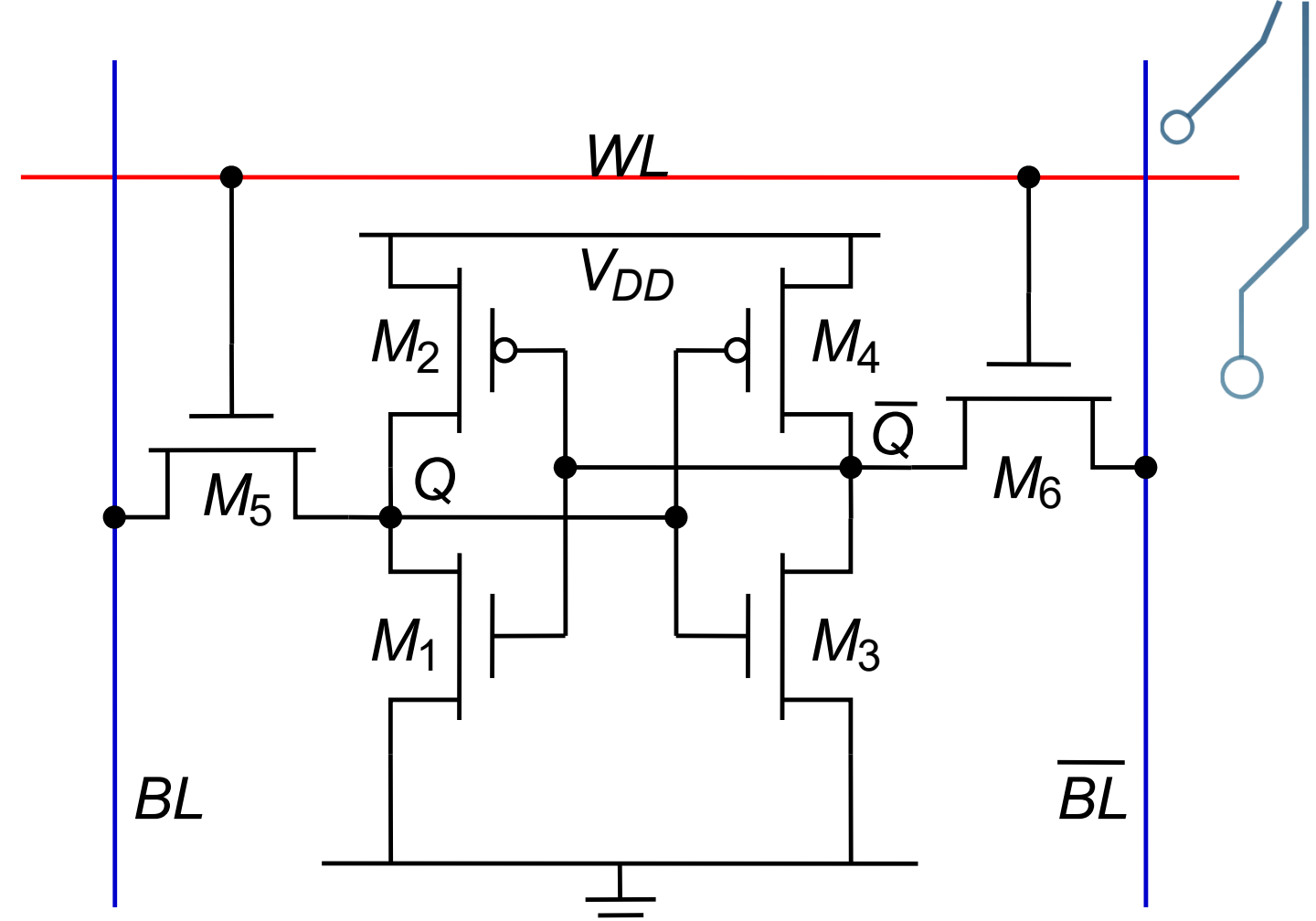- Read stability: Cell should not change value during read
 - $Q = 0$: M_5, M_1 both on
 - Voltage divider between M_5, M_1
 - V_Q should stay low, not to flip M_4 - M_3 inverter
 - $(W/L)_1 > (W/L)_5$
- Typically $(W/L)_1 = 1.5 (W/L)_5$
 - In finFETs: $(W/L)_1 = 2(W/L)_5$
- Read speed: Both M_5 and M_1




Sizing SRAM Cell

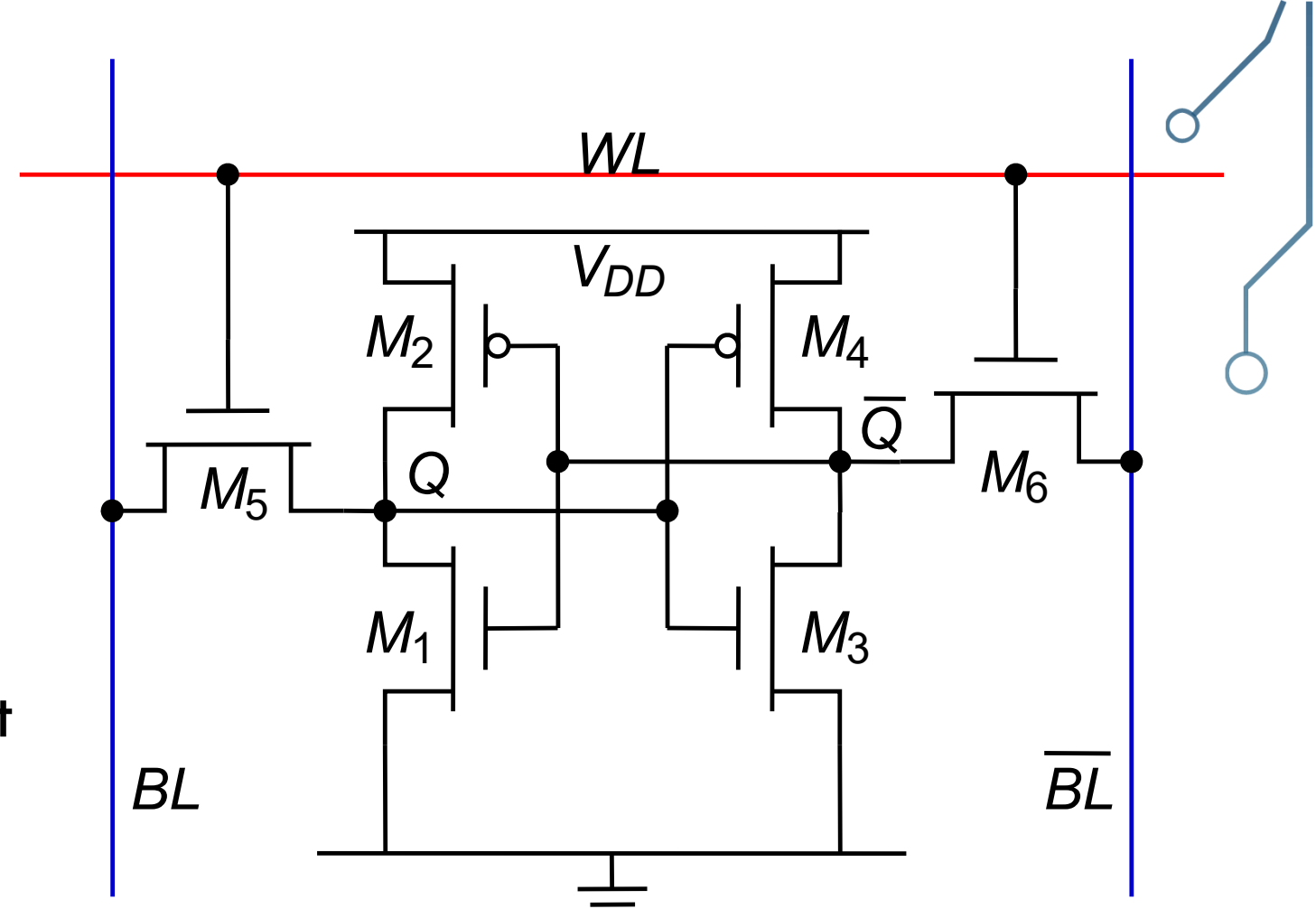- Writeability: Cell should be writeable by pulling BL low
 - $Q = 1$, M_5 , M_2 both on
 - Voltage divider between M_5 , M_2
 - V_Q should pull below the switching point of M_4 - M_3 inverter
 - $(W/L)_5 > (W/L)_2$
- Typically $(W/L)_5 = (W/L)_2$ in planar
 - In finFETs: $(W/L)_5 = 2(W/L)_2$
 - 1:2:2 and 1:2:3 sizing






 
6T High-Current (HC) bitcell
0.049 μm^2 (1:2:2)




Song, ISSCC'16

 A decorative graphic consisting of several vertical lines of varying heights and widths, with small circles at the top and bottom of some lines, resembling a stylized ladder or a series of connected points.



  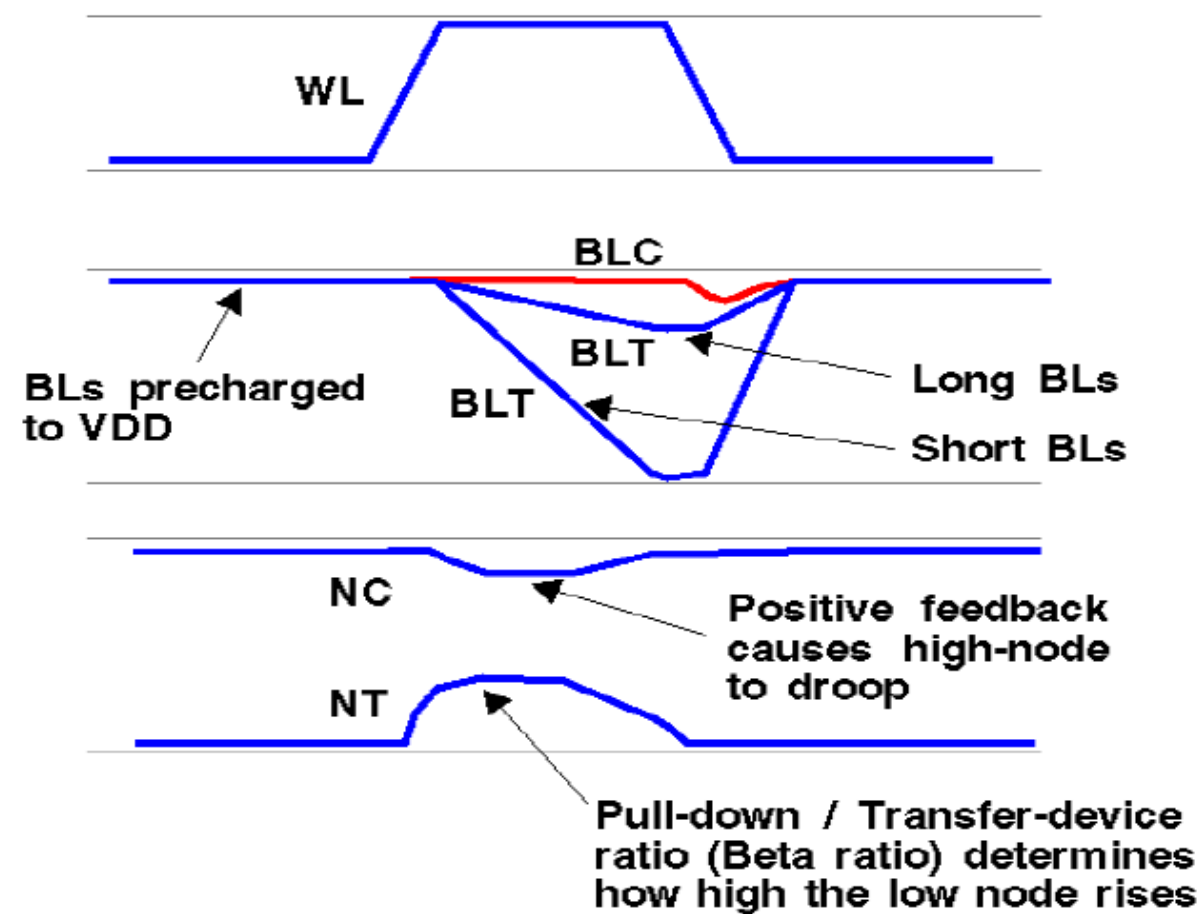[illegible]

SRAM Array Layout

 


R	R	R	R
Б	Б	Б	Б
R	R	R	R
Б	Б	Б	Б

R	Я	R	Я
Б	Я	Б	Я
R	Я	R	Я
Б	Я	Б	Я




Memory Decoders

Decoders

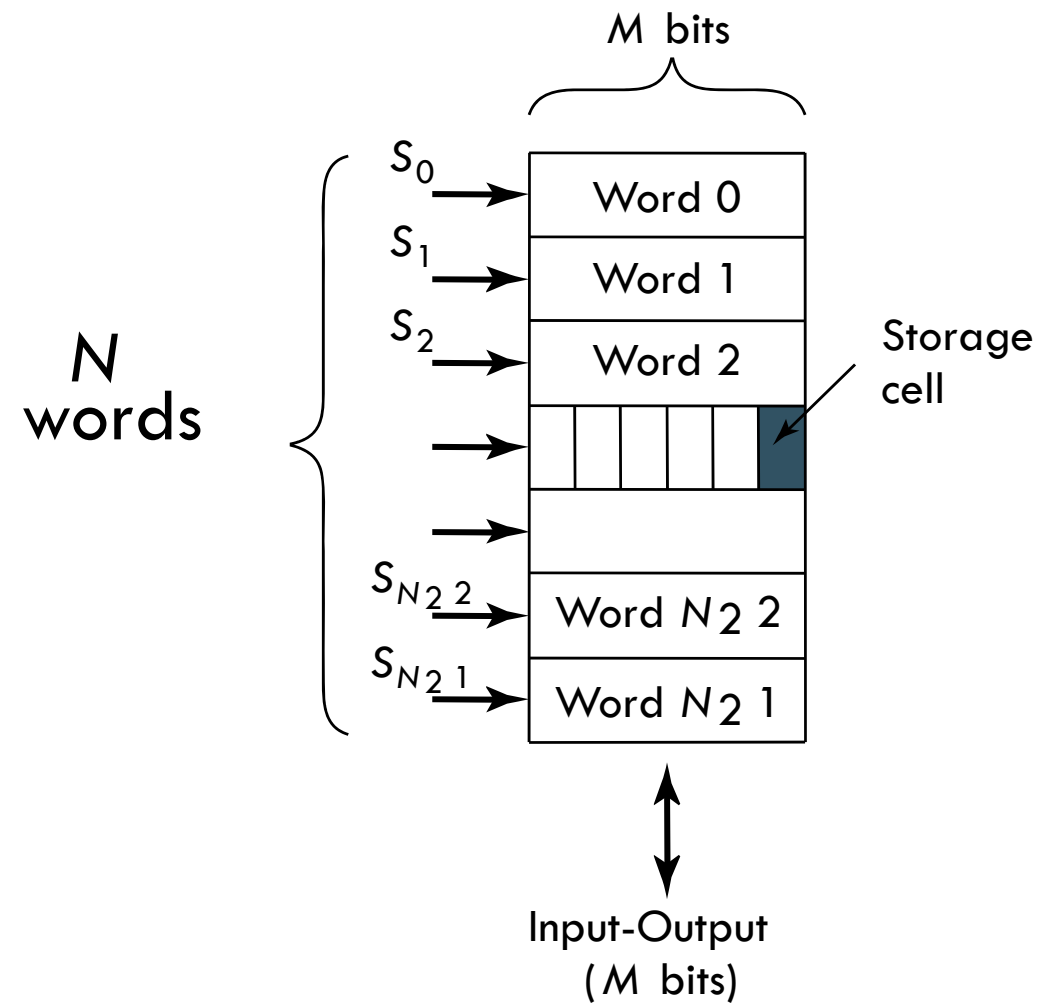

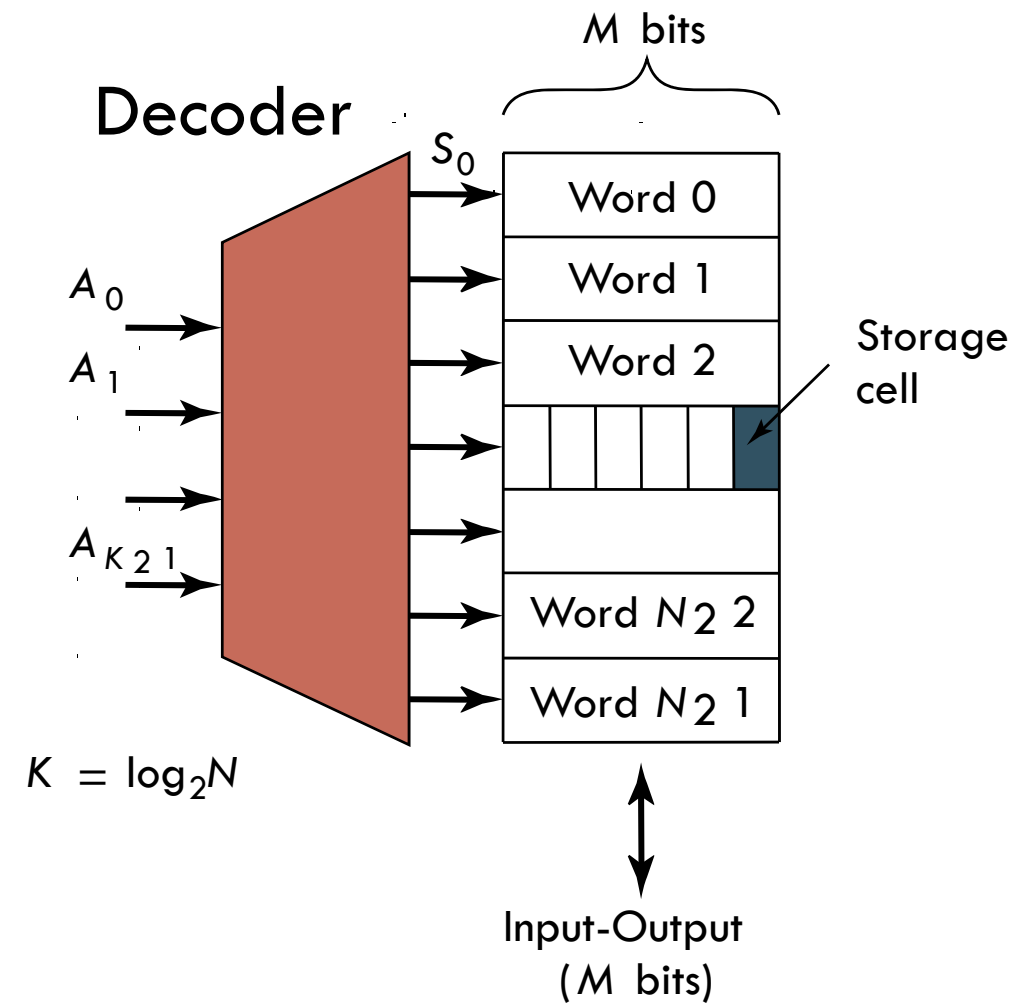Intuitive architecture for $N \times M$ memory
Too many select signals:
 N words = N select signals



Decoder reduces the number of select signals
 $K = \log_2 N$

Row Decoders

Collection of 2^M complex logic gates
Organized in regular and dense fashion

(N)AND Decoder

$$WL_0 = \overline{A_0} \overline{A_1} \overline{A_2} \overline{A_3} \overline{A_4} \overline{A_5} \overline{A_6} \overline{A_7} \overline{A_8} \overline{A_9}$$

$$WL_{511} = A_0 A_1 A_2 A_3 A_4 A_5 A_6 A_7 A_8 \overline{A_9}$$


NOR Decoder

$$WL_0 = \overline{A_0 + A_1 + A_2 + A_3 + A_4 + A_5 + A_6 + A_7 + A_8 + A_9}$$

$$WL_{511} = \overline{\overline{A_0} + \overline{A_1} + \overline{A_2} + \overline{A_3} + \overline{A_4} + \overline{A_5} + \overline{A_6} + \overline{A_7} + \overline{A_8} + A_9}$$


Decoder Design Example

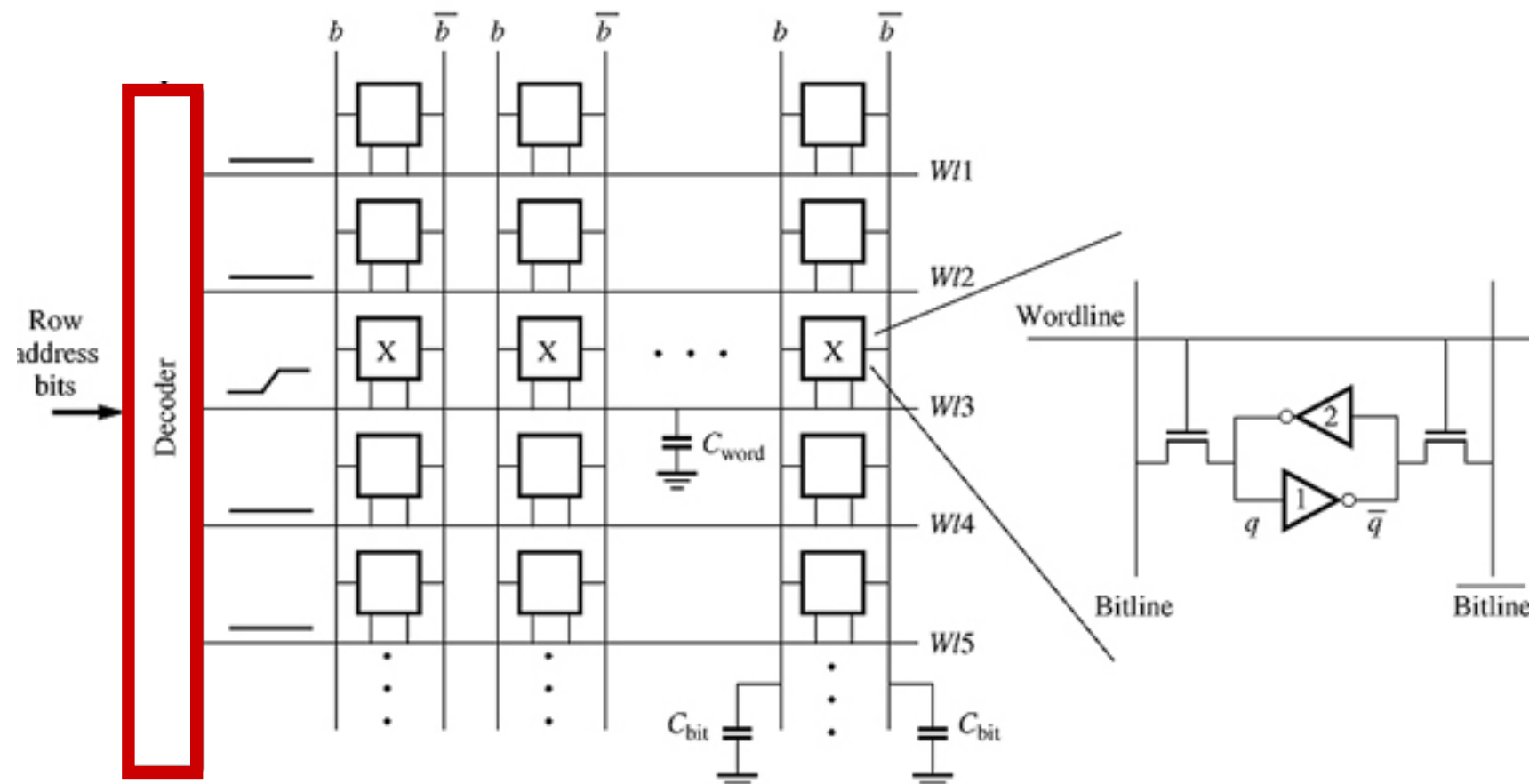- Look at decoder for 256x256 memory block (8KBytes)




Possible Decoder

 - 256 8-input AND gates
 - Each built out of a tree of NAND gates and inverters
- Need to drive a lot of capacitance (SRAM cells)
 - What's the best way to do this?




Possible AND8

 - Build 8-input NAND gate using 2-input gates and inverters
- Is this the best we can do?
- Is this better than using fewer NAND4 gates?



 Problem Setup

- Goal: Build fastest possible decoder with static CMOS logic
- What we know
 - Basically need 256 AND gates, each one of them drives one word line



Problem Setup (1)

- Each wordline has 256 cells connected to it
- $C_{WL} = 256 * C_{cell} + C_{wire}$
 - Ignore wire for now
- Assume that decoder input capacitance is $C_{address} = 4 * C_{cell}$

Problem Setup (2)

- Each address bit drives $2^8/2$ AND gates
 - A0 drives $1/2$ of the gates, A0_b the other $1/2$ of the gates

Problem Setup (3)


- Total fanout on each address wire is:

$$F = \Pi B \frac{C_{load}}{C_{in}} = 128 \frac{(256 C_{cell})}{4 C_{cell}} = 2^7 \frac{(2^8 C_{cell})}{2^2 C_{cell}} = 2^{13}$$

Decoder Fan-Out

- F of 2^{13} means that we will want to use more than $\log_4(2^{13}) = 6.5$ stages to implement the AND8
- Need many stages anyways
 - So what is the best way to implement the AND gate?
 - Will see next that it's the one with the most stages and least complicated gates

8-Input AND

 

$$LE : 9/2 \quad 1$$

$$\Pi LE = 9/2$$

$$P = 8 + 1$$

$$LE : 5/2 \quad 3/2$$

$$\Pi LE = 15/4$$

$$P = 4 + 2$$


$$LE : 3/2 \quad 3/2 \quad 3/2 \quad 1$$

$$\Pi LE = 27/8$$

$$P = 2 + 2 + 2 + 1$$


8-Input AND

 - Using 2-input NAND gates
 - 8-input gate takes 6 stages
- Total LE is $(3/2)^3 \approx 3.4$
- So PE is $3.4 * 2^{13}$ – optimal N of ~ 7.4







Decoder So Far

 - 256 8-input AND gates
 - Each built out of tree of NAND gates and inverters
- Issue:
 - Every address line has to drive 128 gates (and wire) right away
 - Forces us to add buffers just to drive address inputs




Look Inside Each AND8 Gate

    

Predecoders


- Use a single gate for each of the shared terms
 - E.g., from A_0 , $\overline{A_0}$, A_1 , and $\overline{A_1}$, generate four signals: A_0A_1 , $\overline{A_0}A_1$, $A_0\overline{A_1}$, $\overline{A_0}\overline{A_1}$
- In other words, we are decoding smaller groups of address bits first
 - And using the “predecoded” outputs to do the rest of the decoding

Predecoder and Decoder

 

Predecode Options

 - Larger predecode usually better:
- More stages before the long wires
 - Decreases their effect on the circuit
- Fewer number of long wires switches
 - Lower power
- Easier to fit 2-input gate into cell pitch



Review

- Flip-flop is typically a latch pair
- Setup and hold times are defined at constant percentage increases over clk-q delay
- SRAM has unique combination of density, speed, power
- SRAM cells sized for stability and writeability